

A Leading Provider of Microcontroller, Security, Mixed-Signal, Analog & Flash-IP Solutions



***Presented by:
Jake Lee, Senior Embedded Solutions Engineer
May 10, 2018***



Zero-Drift Operational Amplifiers


Architecture Overview and Design Considerations

Agenda

- **Definitions/Architecture**
 - “Precision” amplifiers, “zero-drift” amplifiers
- **Advantages of Zero-Drift Architecture**
 - Versus wafer/package trimmed, calibrated
- **Design Considerations**
 - Input bias and offset currents
 - Noise considerations
 - Thermal drift
 - Output settling/overload recovery
 - Enhanced EMI rejection

Amplifier Definitions


 
- **Input Offset Voltage**
 - Voltage delta between inverting and non-inverting amplifier inputs
- **“Ideal” Op Amp Model**
 - Input offset voltage is zero
- **“Precision” Amplifier**
 - Specifies a maximum offset voltage $<1 \text{ mV}$




What is a Zero-Drift Amplifier?

- **“Zero-Drift” Industry Standard Term**
- **V_{OS} is Continuously Corrected**
- **Two Basic Architectures**
 - Auto-zero
 - Use of a main amplifier and nulling amplifiers to correct offset
 - Chopper-stabilized
 - Use of a main amp and an “auxiliary amp” with chopped inputs/outputs to correct offset

Auto-Zero Architecture

 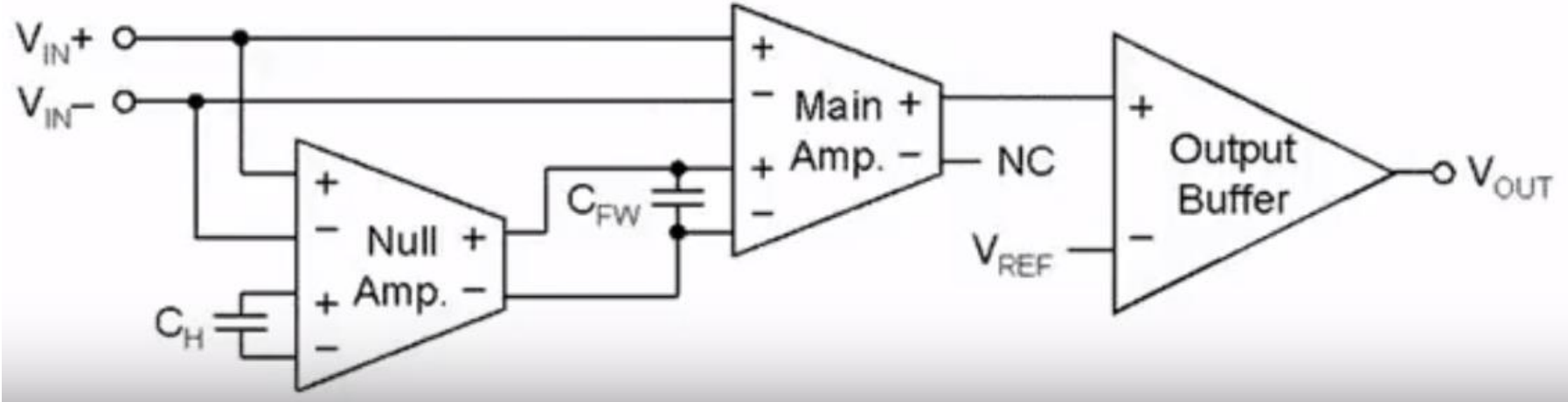

Chopper-Stabilized Architecture

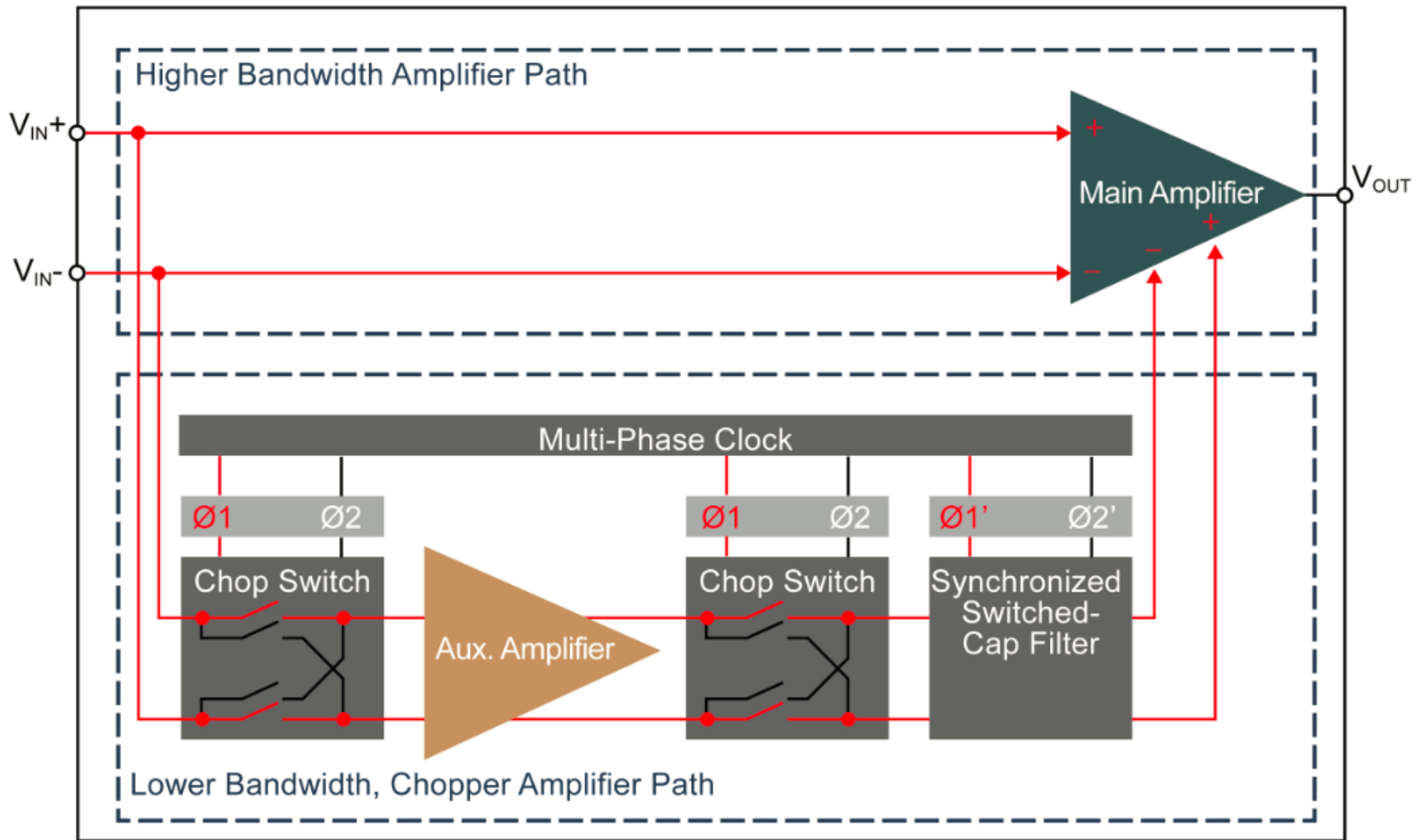

Zero-Drift Amplifiers Advantages/Disadvantages

- **V_{OS} is Corrected Frequently**


- Example, every 10 μs

- **Advantages**

- Accurate (DC up to 400 Hz, or more)
- Insensitive to environment
- V_{OS} aging virtually eliminated
- No user inputs needed


- **Disadvantages**

 - Package size (auto-zero)
- Higher price
- Switching effects



Comparison of Op Amp Architectures

● Offset Aging

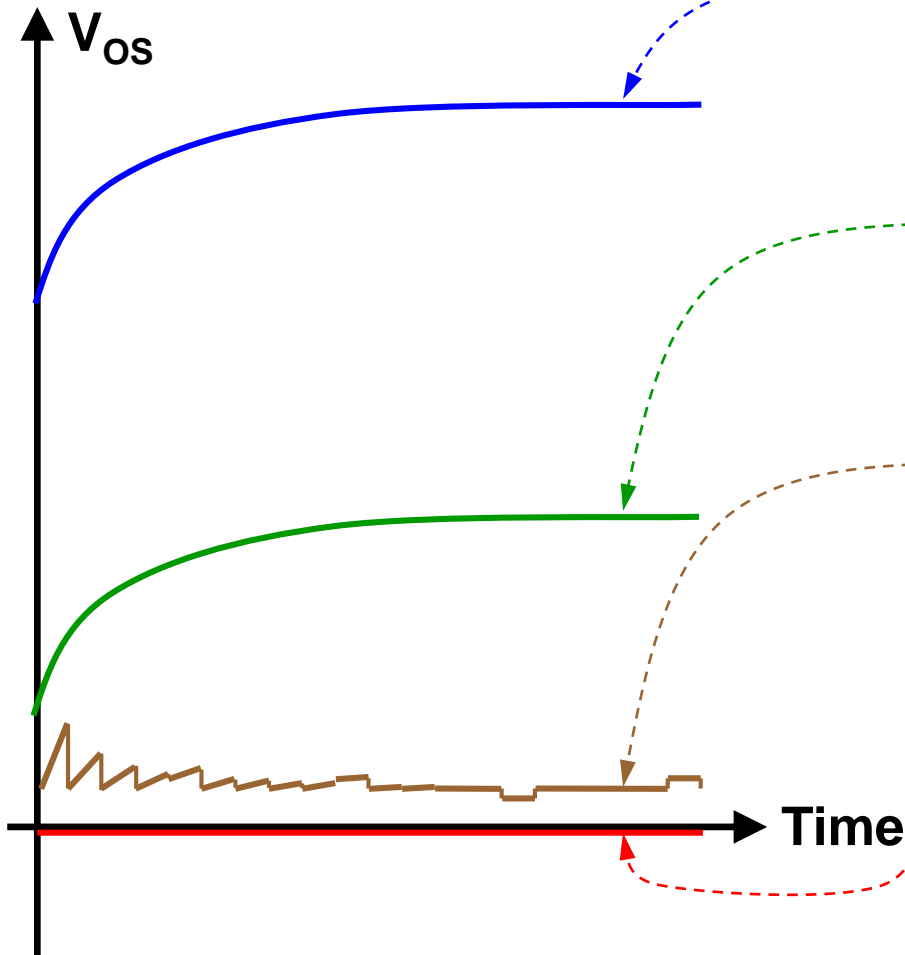

General Purpose

$V_{OS} < \pm 3000 \mu V$ (typ.)

V_{OS} aging $< \pm 300 \mu V$ (typ.)

EPROM Trimmed

$V_{OS} < \pm 250 \mu V$ (typ.)

V_{OS} aging $< \pm 300 \mu V$ (typ.)

Calibrated (mCal)

$V_{OS} < \pm 200 \mu V$ (typ.)

V_{OS} aging $< \pm 50 \mu V$ (typ.)

V_{OS} repeatability $< \pm 50 \mu V$ (typ.)


Zero-Drift

$V_{OS} < \pm 3 \mu V$ (typ.)

V_{OS} aging $< \pm 1 \mu V$ (typ.)


Comparison of Op Amp Architectures

• Offset Drift (over Temperature)

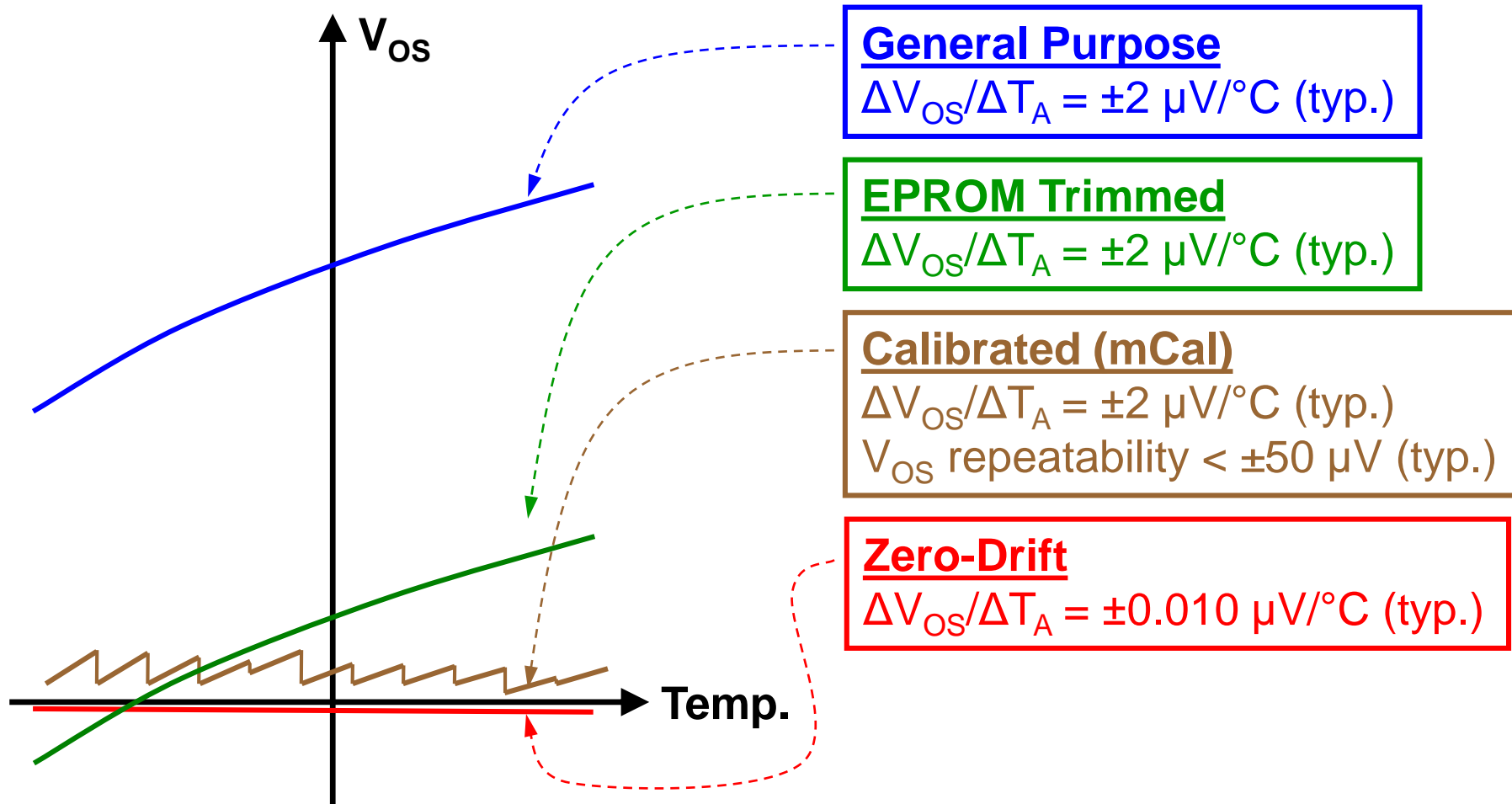

Comparison of Op Amp Architectures

• Offset Changes due to Bias Condition

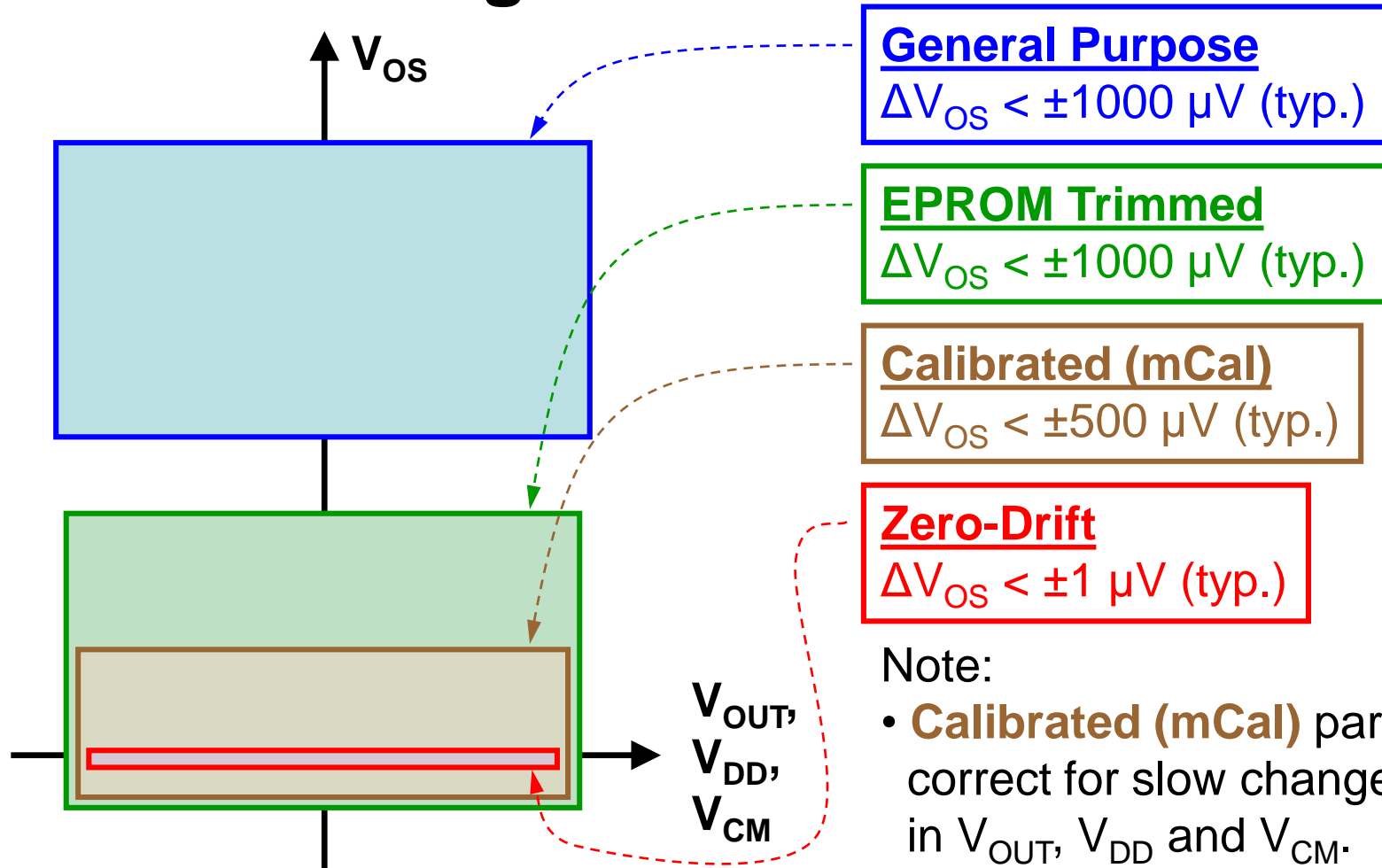

Example Comparison: General Purpose VS Zero-Drift

Part #		MCP6401	MCP6V61	
Family		General Purpose	Zero-Drift	
GBWP (MHz)		1	1	
Specified Op Voltage (V)		1.8 to 6.0	1.8 to 5.5	
Max Vos (μV)		4500	8	560x Better!
Vos Drift ($\mu\text{V}/^\circ\text{C}$)		2 (typ)	0.015	130x Better!
Typ CMRR (dB)		76	128	400x Better!
Typ PSRR (dB)		78	134	630x Better!
Noise (nV/ $\sqrt{\text{Hz}}$) @ 1kHz		28	26	
Iq (μA)	Typical	45	80	
	Max	70	130	

Zero-Drift Application Examples

- **Weight scales**
- **Oxygen sensor**
- **Temperature transmitter**
- **Methane detector**
- **Fire detection**
- **Lighting**
- **Flow meters**
- **Alcohol tester**
- **Thermocouple isolator**
- **Current sensor**
- **Appliances**
- **Cryogenics**
- **Power supplies**
- **Gas meters**




Zero-Drift Operational Amplifiers

Design Considerations



Input Bias and Offset Current

 - **Two Physical Currents at the Input Pins**
- **Flow Into the Device is Positive, Flow Out of the Device is Negative**



Input Bias/Offset Current Definitions

- **Input Bias Current:**

$$I_B = \frac{I_{B_N} + I_{B_I}}{2}$$


- **Input Offset Current:**

$$I_{OS} = I_{B_N} - I_{B_I}$$

- **Rearranging:**

$$I_{B_N} = I_B + \frac{I_{OS}}{2}$$

$$I_{B_I} = I_B - \frac{I_{OS}}{2}$$

 


Input Bias/Offset Current Example

● MCP6V06 Zero-Drift Op Amp

Input Bias Current and Impedance

Input Bias Current	I_B	—	+6	—	pA
Input Bias Current across Temperature	I_B	—	+140	—	pA
	I_B	—	+1500	+5000	pA
Input Offset Current	I_{OS}	—	-85	—	pA

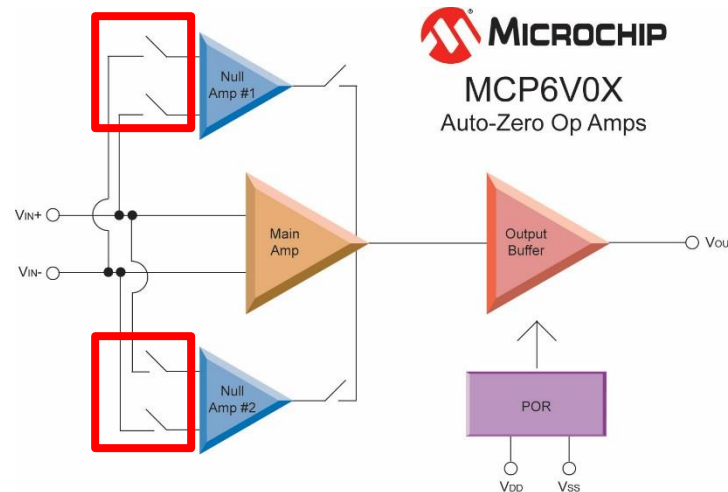


Input Bias/Offset Current Example

- **MCP6V06 Leakage Currents**

$$I_{B_N} = -37 \text{ pA}$$

$$I_{B_I} = +49 \text{ pA}$$

 


- **Summary**

- For traditional amplifiers, I_{OS} is small
- For zero-drift, may factor into error budget

Noise Considerations: 1/f Noise


- Also known as “flicker” noise, caused by stray currents on the silicon substrate
- Inherent to all silicon based electronics
- Dominate noise source at low frequency
- Zero-drift architecture eliminates 1/f noise as part of the offset correction

Noise Profiles by Architecture

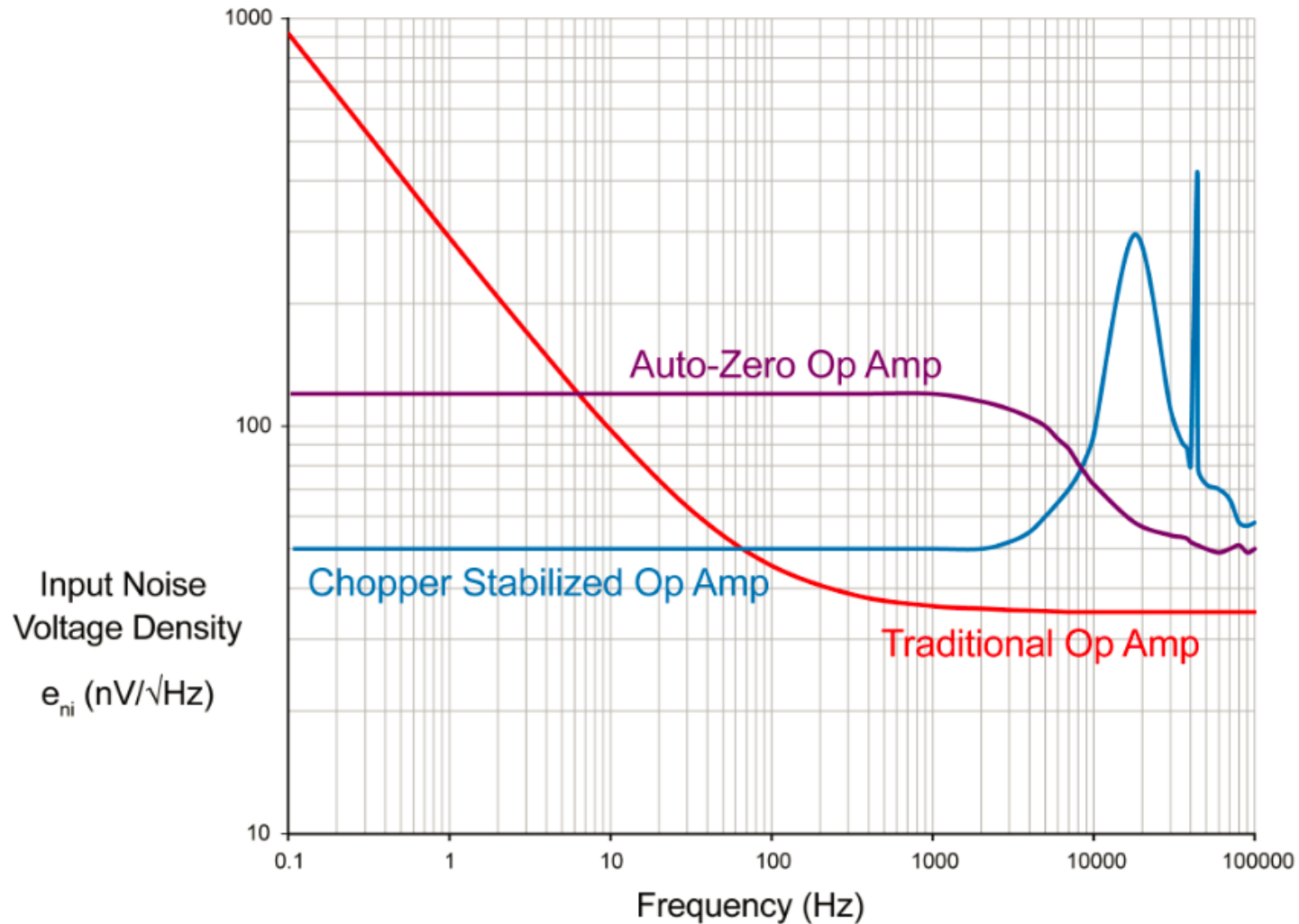


Noise Profile

1) Traditional Op Amp

 


Noise Profile

2) Auto-Zero Op Amp

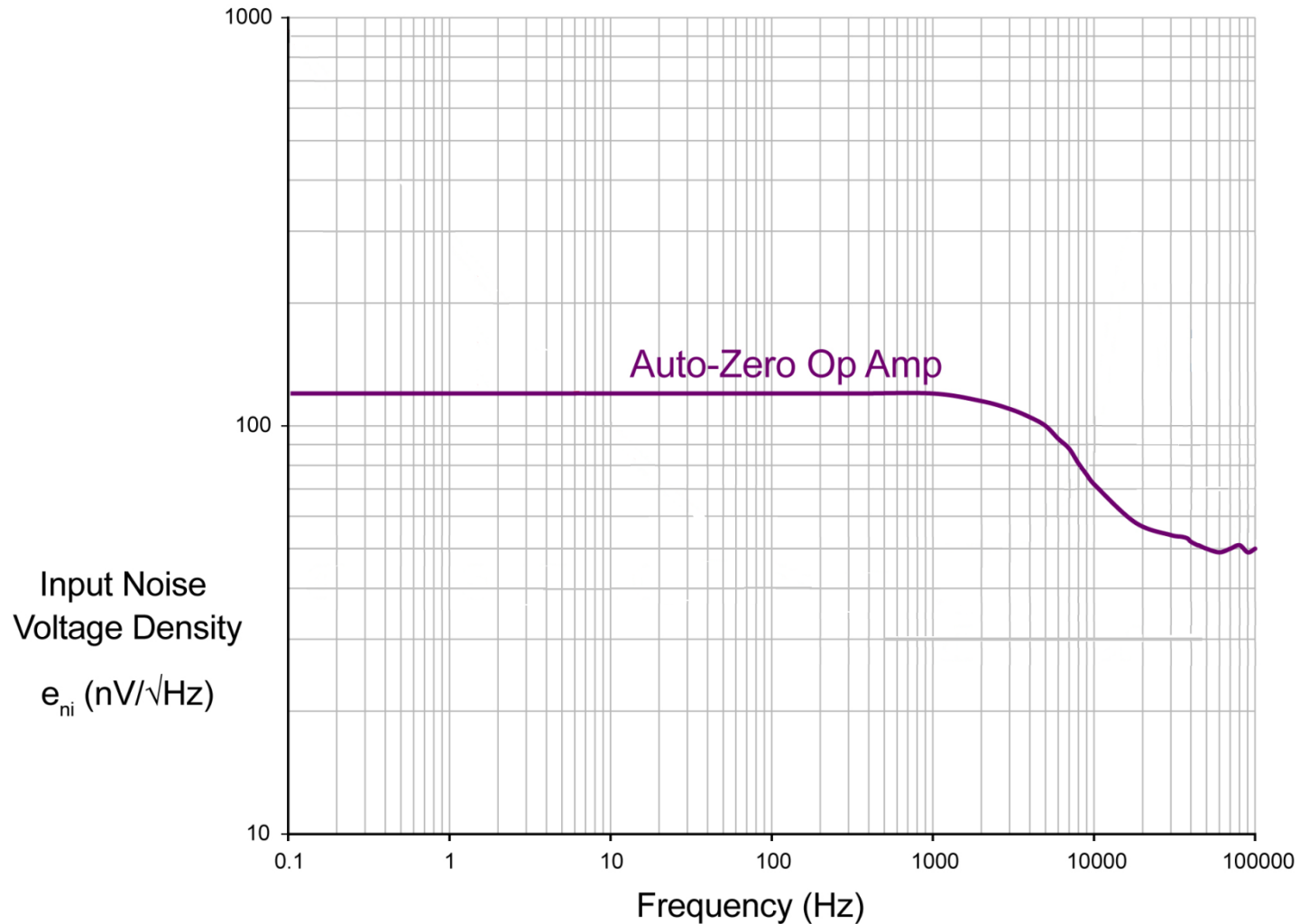


Noise Profile

3) Chopper Op Amp

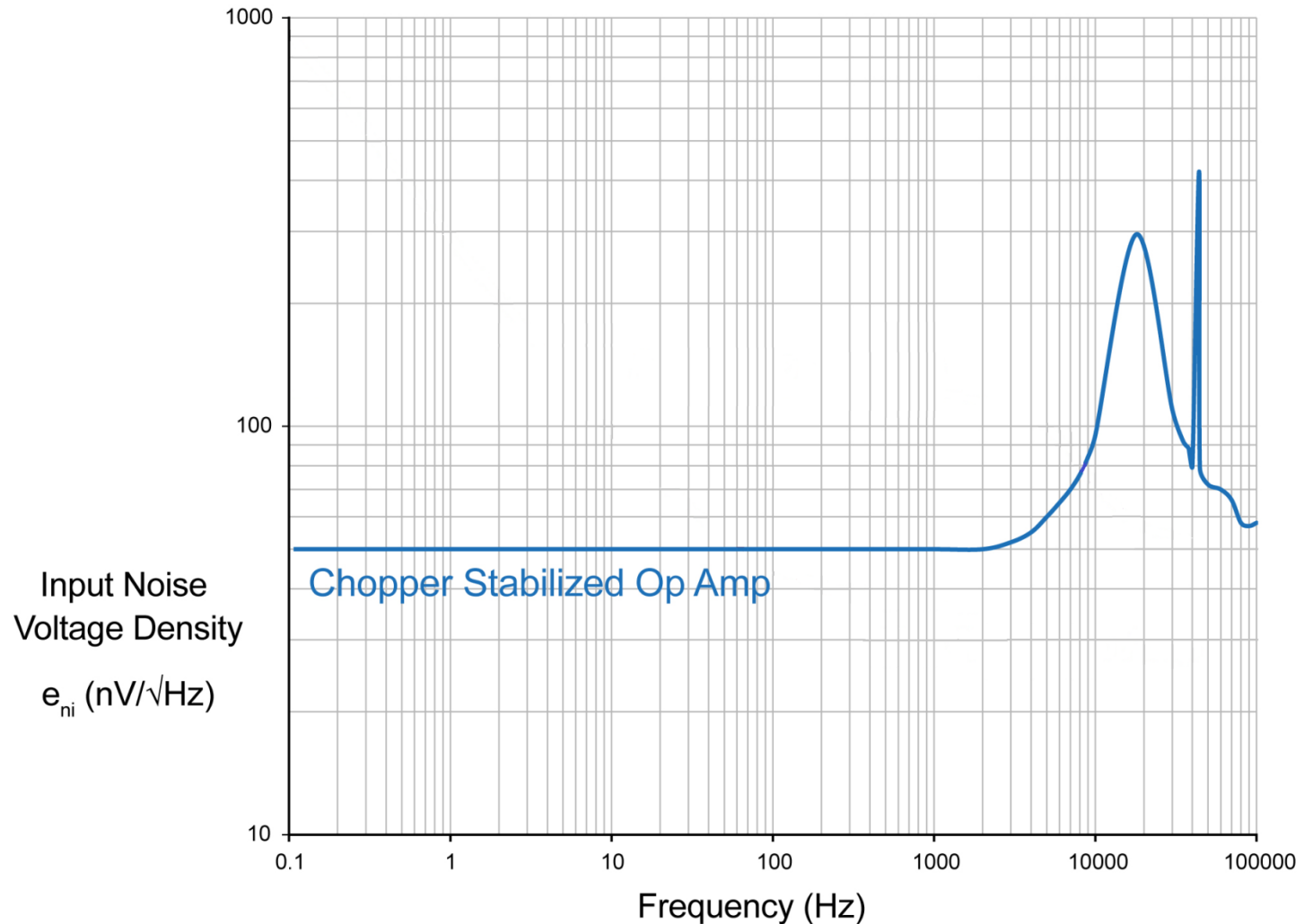

1/f Noise Summary

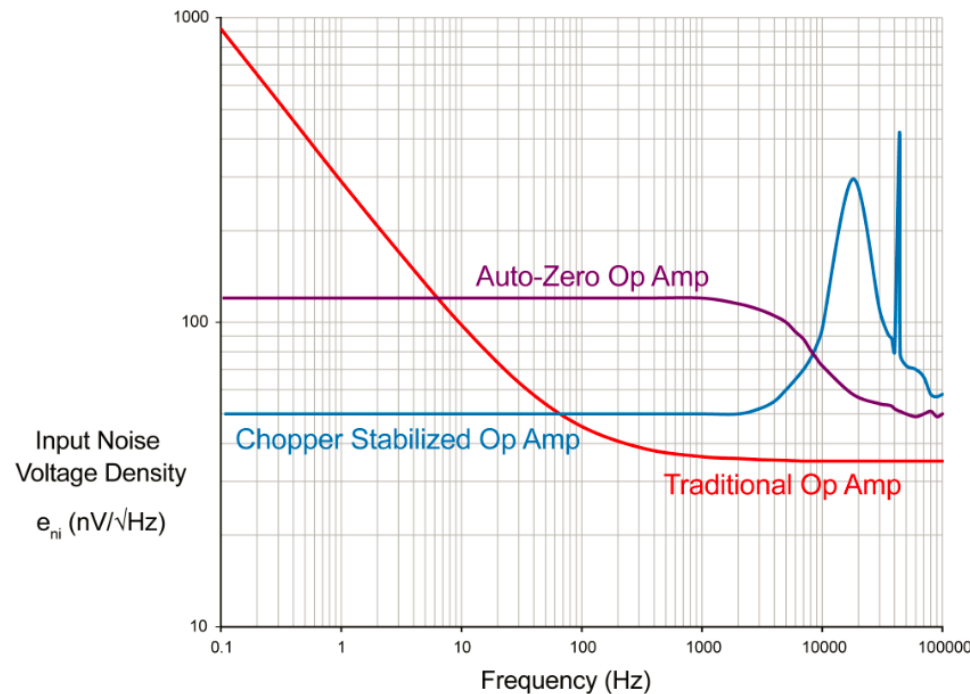- Zero-drift architecture eliminates 1/f
- Chopper is lower noise, noise peaking
- Auto-zero, noise folded into baseband




Noise Considerations: Voltage and Current Noise

- **When discussing noise, voltage noise tends to be the first consideration**
- **Current noise can also be a factor**
- **Definitions**
 - Voltage noise: Internal voltage noise of the amplifier that is reflected back to an ideal voltage source in parallel with the input pins
 - Current noise: Internal current noise of the amplifier that is reflected back to an ideal current source in parallel with the input pins

Noise Considerations: Voltage and Current Noise

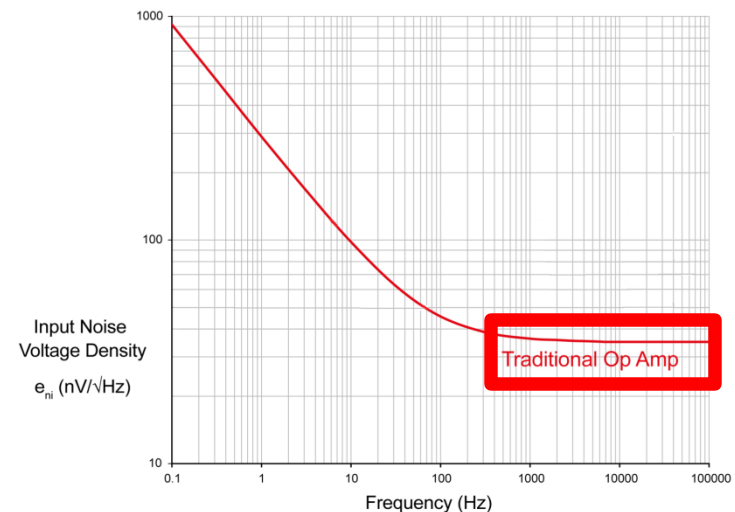- **Noise has power spectrum:**
 - Voltage noise: $\text{nV}/\sqrt{\text{Hz}}$
 - Current noise: $\text{pA}/\sqrt{\text{Hz}}$
- **Specified where the white noise of the amplifier dominates**
 - Eliminates any $1/f$ noise effects



Voltage and Current Noise Application Example

- **Application example**
 - Two precision amplifiers available on the market today


Parameters	Op Amp A	Op Amp B
Max Input Offset Voltage (μV)	200	500
GBWP (MHz)	20	22
Supply Voltage Range (V)	2.5-5.5	1.8-5.5
Voltage Noise Density ($\text{nV}/\sqrt{\text{Hz}}$)	13	2.9
Current Noise Density ($\text{fA}/\sqrt{\text{Hz}}$)	4	1100

- Similar in speed, operating voltage, but noise varies considerably

Voltage and Current Noise Application Example


- **Voltage follower circuit**

 - Amplifier noise
- Input resistor noise
 - $V_{TH} = \sqrt{4kTRB}$



Voltage and Current Noise Application Example


- **Case 1: Input resistance is 0Ω**

 

Noise Source (nV/ $\sqrt{\text{Hz}}$)	Op Amp A	Op Amp B
Amplifier Voltage Noise	13	2.9
Amplifier Current Noise	0	0
Thermal Noise of R_{IN}	0	0
Total Noise	13	2.9

Voltage and Current Noise Application Example


- **Case 2: Input resistance is 10 k Ω**

 

Noise Source (nV/ $\sqrt{\text{Hz}}$)	Op Amp A	Op Amp B
Amplifier Voltage Noise	13	2.9
Amplifier Current Noise	0.04	11
Thermal Noise of R_{IN}	13	13
Total Noise	18	17

Voltage and Current Noise Application Example

 - **Case 3: Input resistance is 100 k Ω**



Noise Source (nV/ $\sqrt{\text{Hz}}$)	Op Amp A	Op Amp B
Amplifier Voltage Noise	13	2.9
Amplifier Current Noise	0.4	110
Thermal Noise of R_{IN}	41	41
Total Noise	43	117

Voltage and Current Noise Summary

- **Both voltage and current noise must be considered**
- **Independent of amplifier architecture**
- **Especially true for high impedance applications**
 - pH meters, oven oscillators, thermocouple circuitry (isolation)

Minimizing Thermal Drift

- **Terminology “Zero-Drift”**
 - Although never actually “zero”, extremely low relative to non zero-drift architectures
 - On the order of 100x better
- **Precision circuitry requires other components (including passives) to also be low drift**
 - Highly dependent on PCB layout


Minimizing Thermal Drift

- **Thermo-junctions**


- Two dissimilar metals come into contact
- Creates a temperature dependent voltage shift

- **Common to PCBs**

 
- Components soldered to copper pads
- Jumpers
- Vias



 
Minimizing Thermal Drift Application Example




Schematic: non-inverting gain

 

Case 1: Worst layout for drift

 

Case 2: Better layout for drift

 


Case 3: Best layout for drift

Minimizing Thermal Drift Summary

- **Selecting precision, low drift ICs not enough**
- **Thermo-junctions create voltage shifts that are dependent on temperature transients**
- **Proper PCB layout can minimize the adverse effects of thermo-junctions**

Output Settling/Overload Recovery Time

 - Large scale step responses or overload conditions are difficult for Zero-Drift Amplifiers
- Two signal paths:
 - High bandwidth path (GBW, slew rate)
 - Lower bandwidth chopper path



Electromagnetic Interference (EMI)


- **Benefits of EMI enhanced amplifiers:**
 - Reduced dependence on external filtering
 - Maintain signal integrity with fewer components
 - Reduction of development time and component cost
 - Specified performance requires good PCB layout and component selection

MCP6V7x EMI enhanced amplifier data sheet:




EMI Rejection Ratio	EMIRR	—	75	—	dB	$V_{IN} = 0.1 V_{PK}, f = 400 \text{ MHz}$
		—	89	—		$V_{IN} = 0.1 V_{PK}, f = 900 \text{ MHz}$
		—	96	—		$V_{IN} = 0.1 V_{PK}, f = 1800 \text{ MHz}$
		—	98	—		$V_{IN} = 0.1 V_{PK}, f = 2400 \text{ MHz}$

EMI Rejection Microchip vs. Competition

 - Microchip second order “RC” architecture for EMI protection



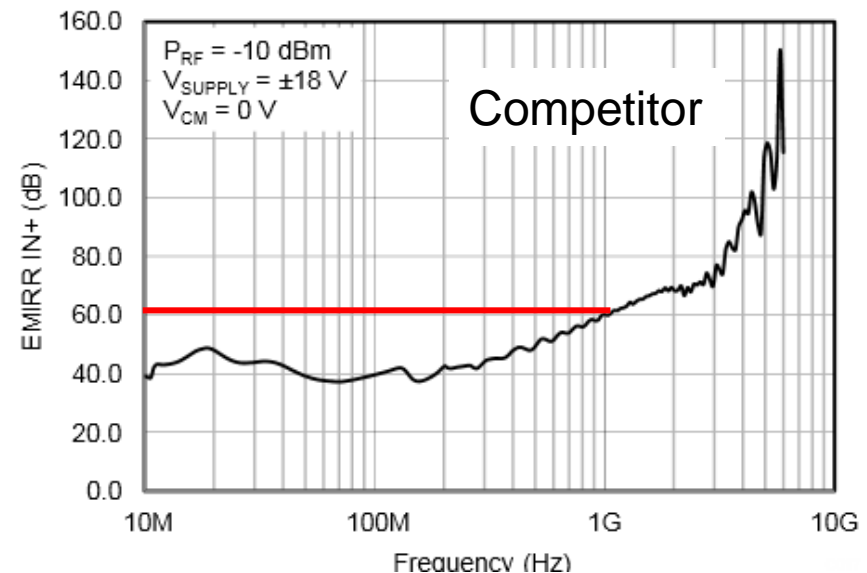  - Simple “RC” architecture for EMI protection



Zero-Drift Amplifiers Summary

- **Zero-Drift Architecture: continuously self-correcting offset voltage errors**
 - Inherent benefits:
 - Low initial offset, low offset drift, eliminates 1/f noise, excellent common mode/power supply rejection
 - Design considerations:
 - Input bias currents, noise, drift, output behavior, susceptibility to EMI



Thank You
