


직류전원 공급기를 통한 전원 인가 및 소모 시험의 난점 및 해결책

최 대류 부장

기술지원 부문/ 파워 스페셜리스트

한국 애질런트 테크놀로지스

Agenda

- The need for source-sink solutions for testing bidirectional and regenerative power devices 
- Solutions to address this need
 - Non-overlapping source-sink solution with Deadband
 - Overlapping source-sink solution
 - Integrated source-sink solution
- New technologies for enabling integrated source-sink solution
- Conclusion

The Need for High Power Sourcing and Sinking

To test high power bidirectional and regenerative energy systems and devices

Host Device:


- Satellites
- Electric mobility
- Robotics
- UPSs
- Green energy systems

Bidirectional and regenerative energy systems and devices:

- Rechargeable batteries
- Super capacitors
- Motor-generators
- Bidirectional DC/DC converters
- Battery management systems (BMS)
- Regenerative braking


Two-Quadrant vs. Four-Quadrant Source Operation

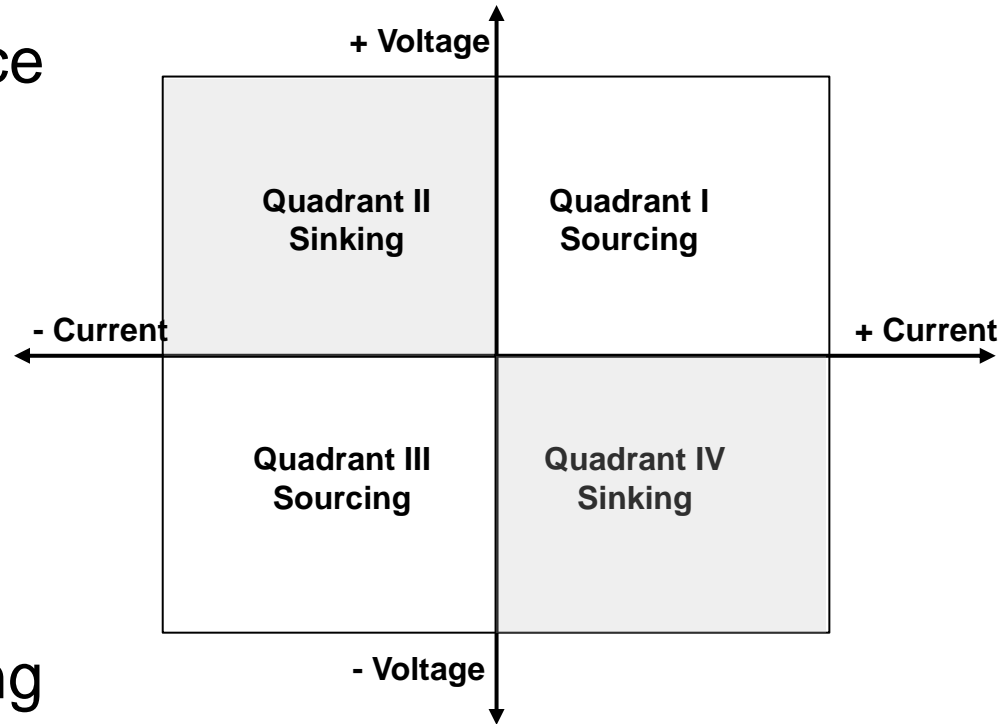- Bidirectional vs. bipolar
- Unipolar, bidirectional source (two-quadrant)
- Bipolar source (four-quadrant)
- Typically two-quadrant operation is needed for testing bidirectional and regenerative power devices




The Need for High Power Sourcing and Sinking

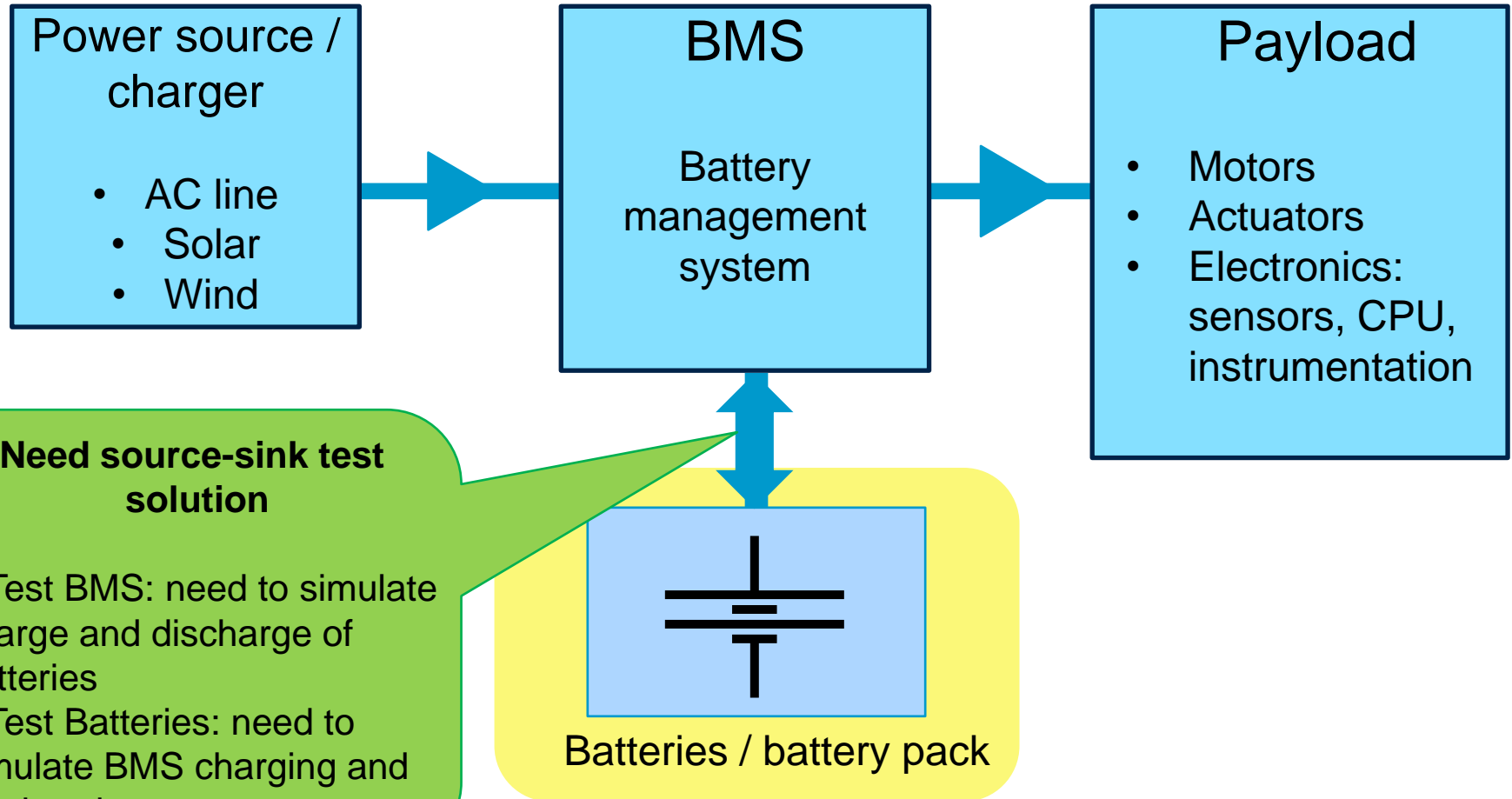Example battery powered device showing power flow



Agenda


- The need for source-sink solutions for testing bidirectional and regenerative power devices
- Solutions to address this need 
 - Non-overlapping source-sink solution with Deadband
 - Overlapping source-sink solution
 - Integrated source-sink solution
- New technologies for enabling integrated source-sink solution
- Conclusion

Source-Sink Solution Requirements

- Two-quadrant solution that can seamlessly transition between sourcing and sinking current
- The ability to operate in CV and CC mode (for testing batteries)
- The ability to handle various load / DUT impedance conditions
- Protection features, limit settings, and fast reaction to questionable test conditions
- Reasonable output noise, accuracy levels, size, and weight


Meeting all these requirements is not easy to find in a single integrated solution

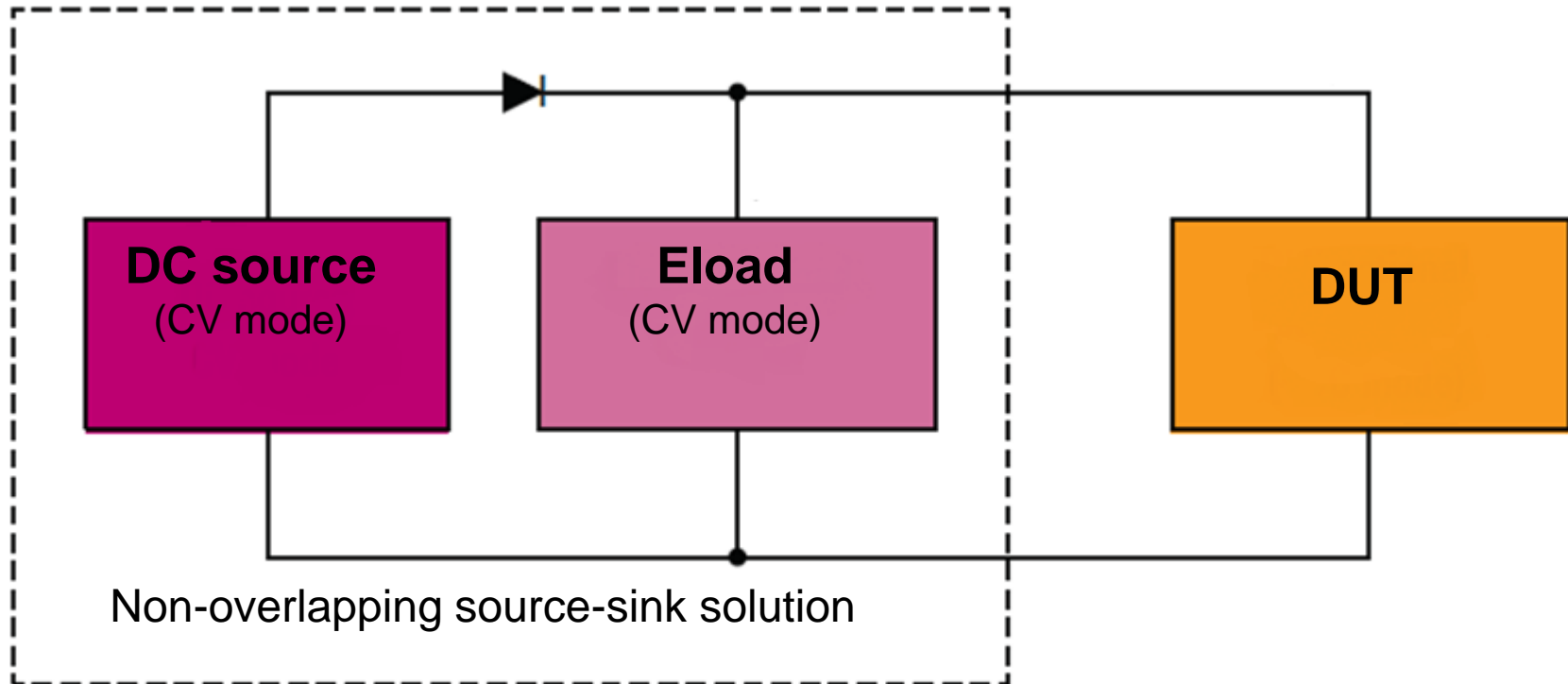Non-Overlapping Source-Sink Solution with Deadband




- This solution uses DC source, electronic load, and diode
- This solution is more suitable for BMS testing, battery testing is challenging with this solution


Sensing

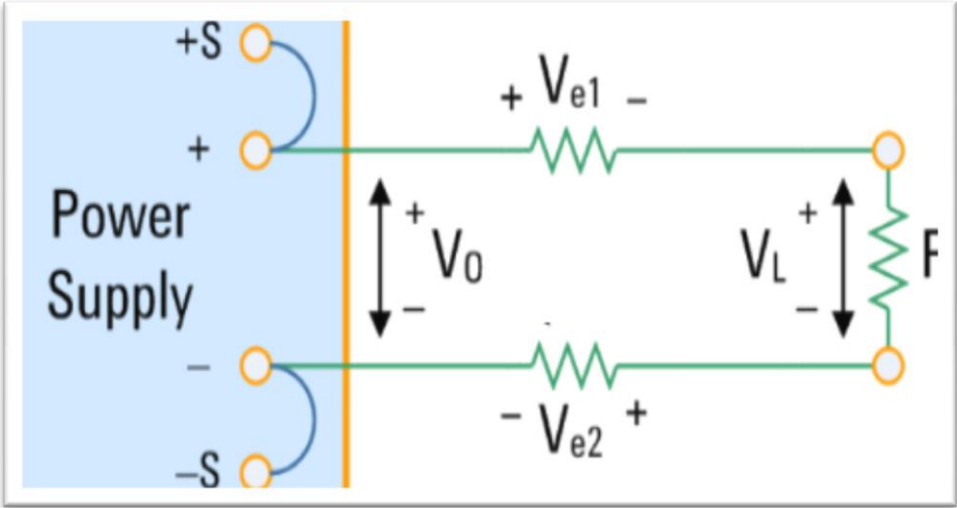

Local Sensing

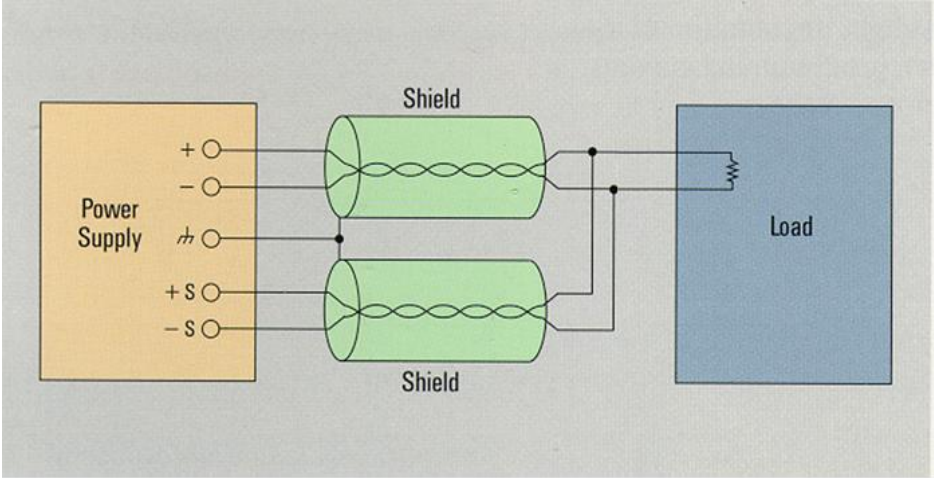


Remote Sensing

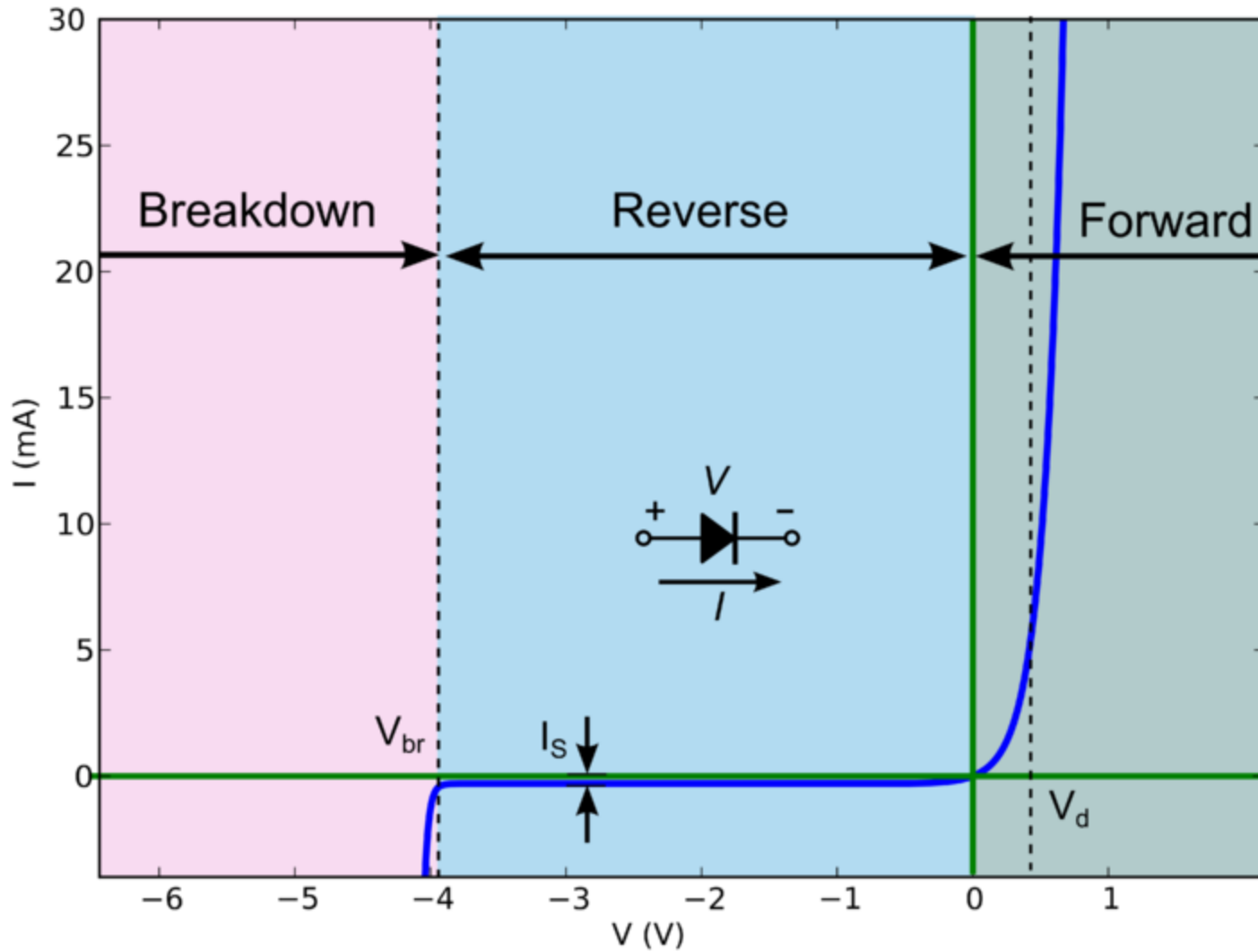

Non-Overlapping Source-Sink Solution with Deadband

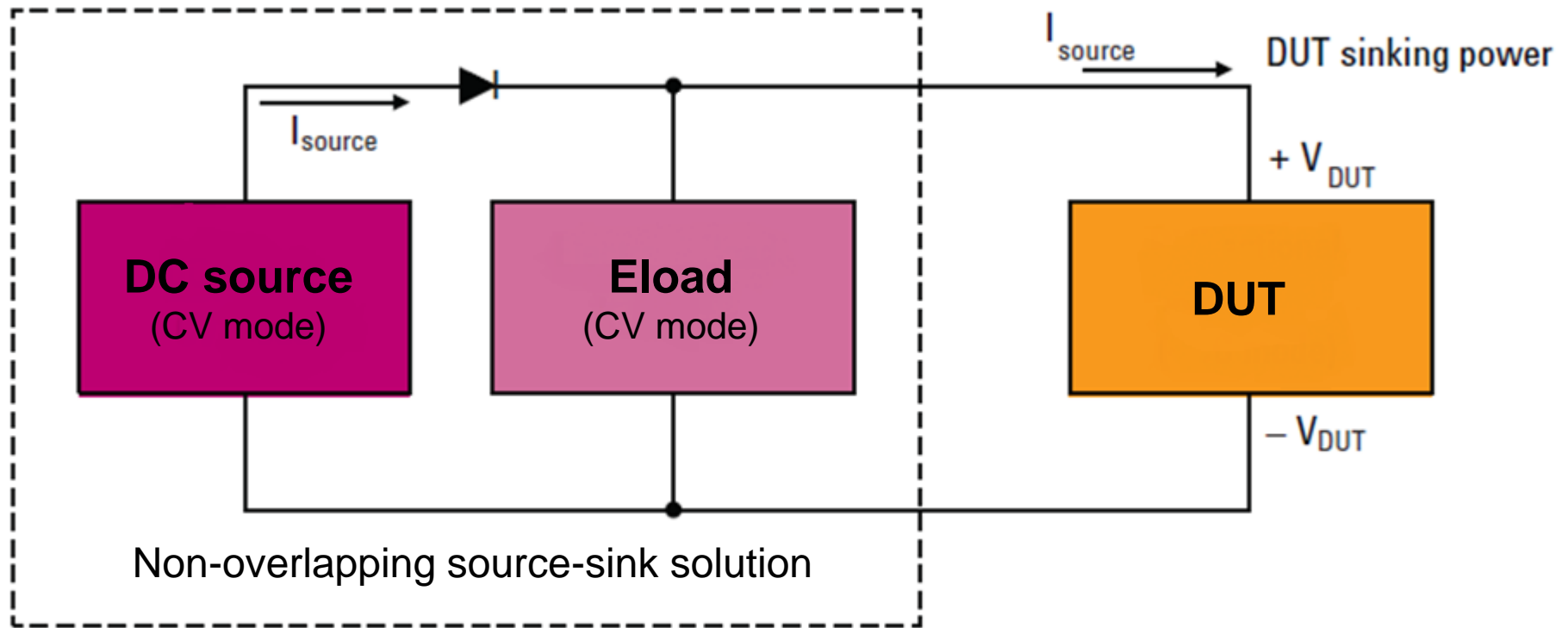
Deadband solution sourcing power, DUT sinking power



- $V_{load} > (V_{source} - V_{diode})$
- DUT sinking power, DC source active: $V_{DUT} = (V_{source} - V_{diode})$
- Eload is in cutoff so it acts like an open

Non-Overlapping Source-Sink Solution with Deadband

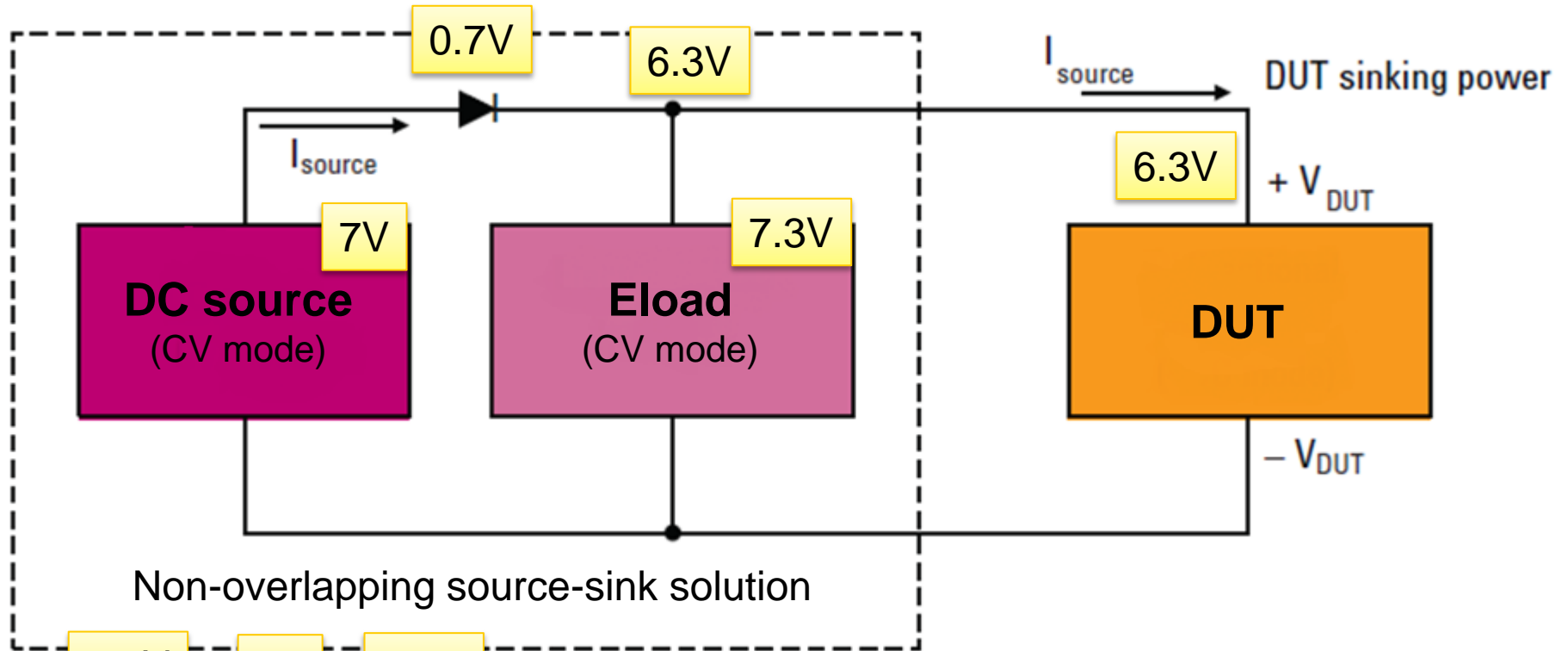
Deadband solution sourcing power, DUT sinking power



- $V_{load} > (V_{source} - V_{diode})$
- DUT sinking power, DC source active: $V_{DUT} = (V_{source} - V_{diode})$
- Eload is in cutoff so it acts like an open

Non-Overlapping Source-Sink Solution with Deadband

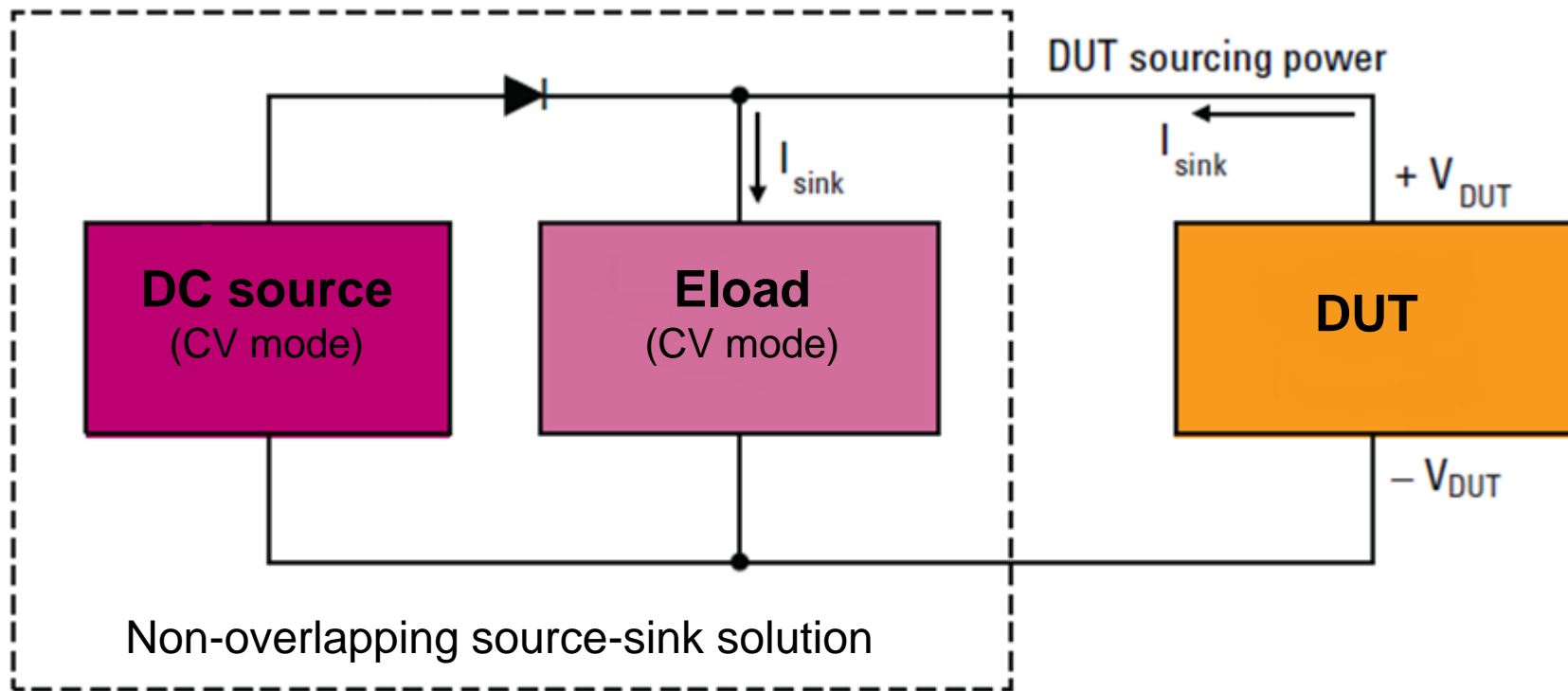
Deadband solution sinking power, DUT sourcing power



- $V_{eload} > (V_{source} - V_{diode})$
- DUT sourcing power, eload active: $V_{DUT} = V_{eload}$
- Diode is reversed biased no current flowing out of DC source

Non-Overlapping Source-Sink Solution with Deadband

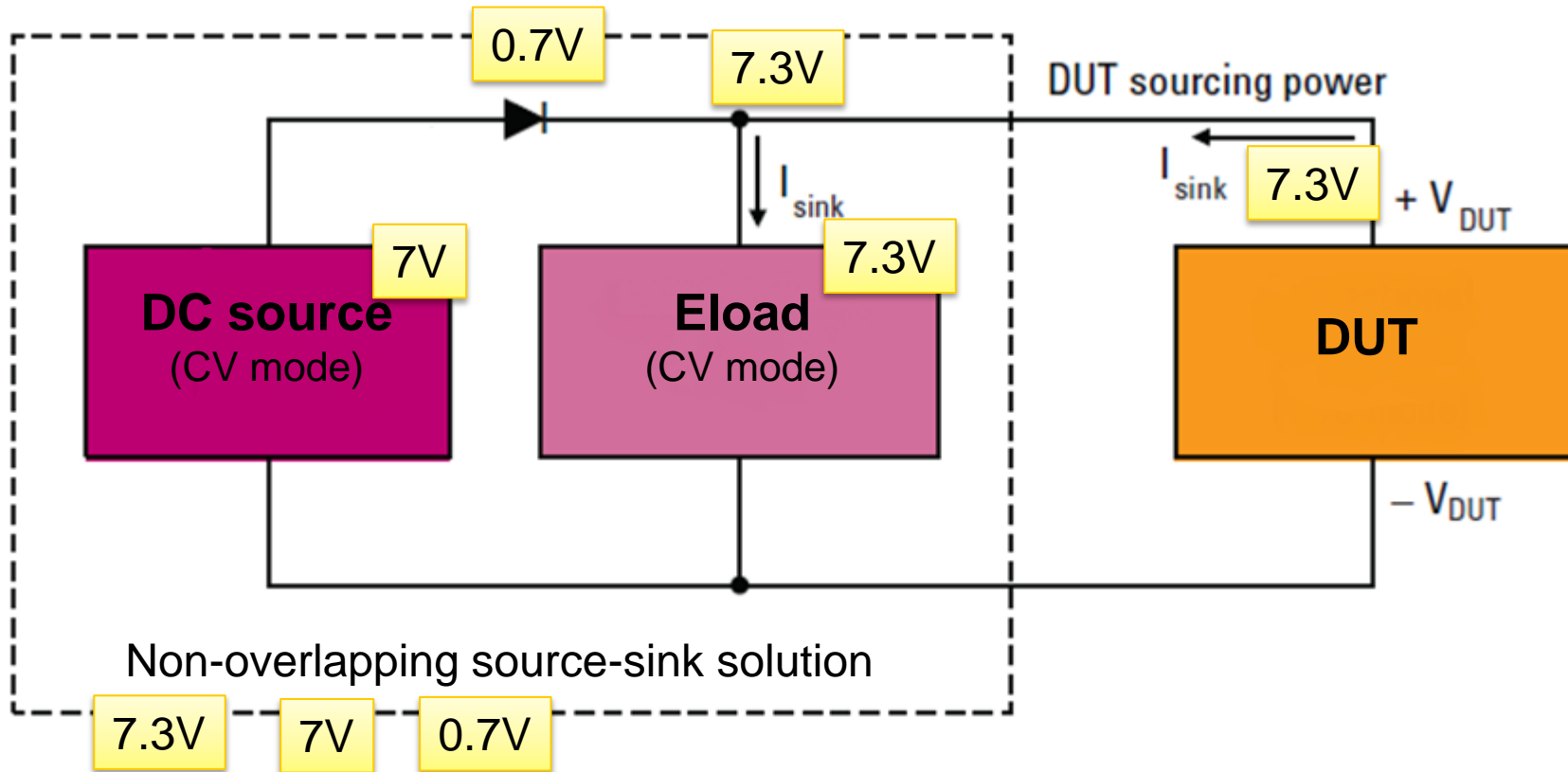
Deadband solution sinking power, DUT sourcing power



- $V_{eload} > (V_{source} - V_{diode})$ 7.3V 7.3V
- DUT sourcing power, eload active: $V_{DUT} = V_{eload}$
- Diode is reversed biased no current flowing out of DC source

Non-Overlapping Source-Sink Solution with Deadband

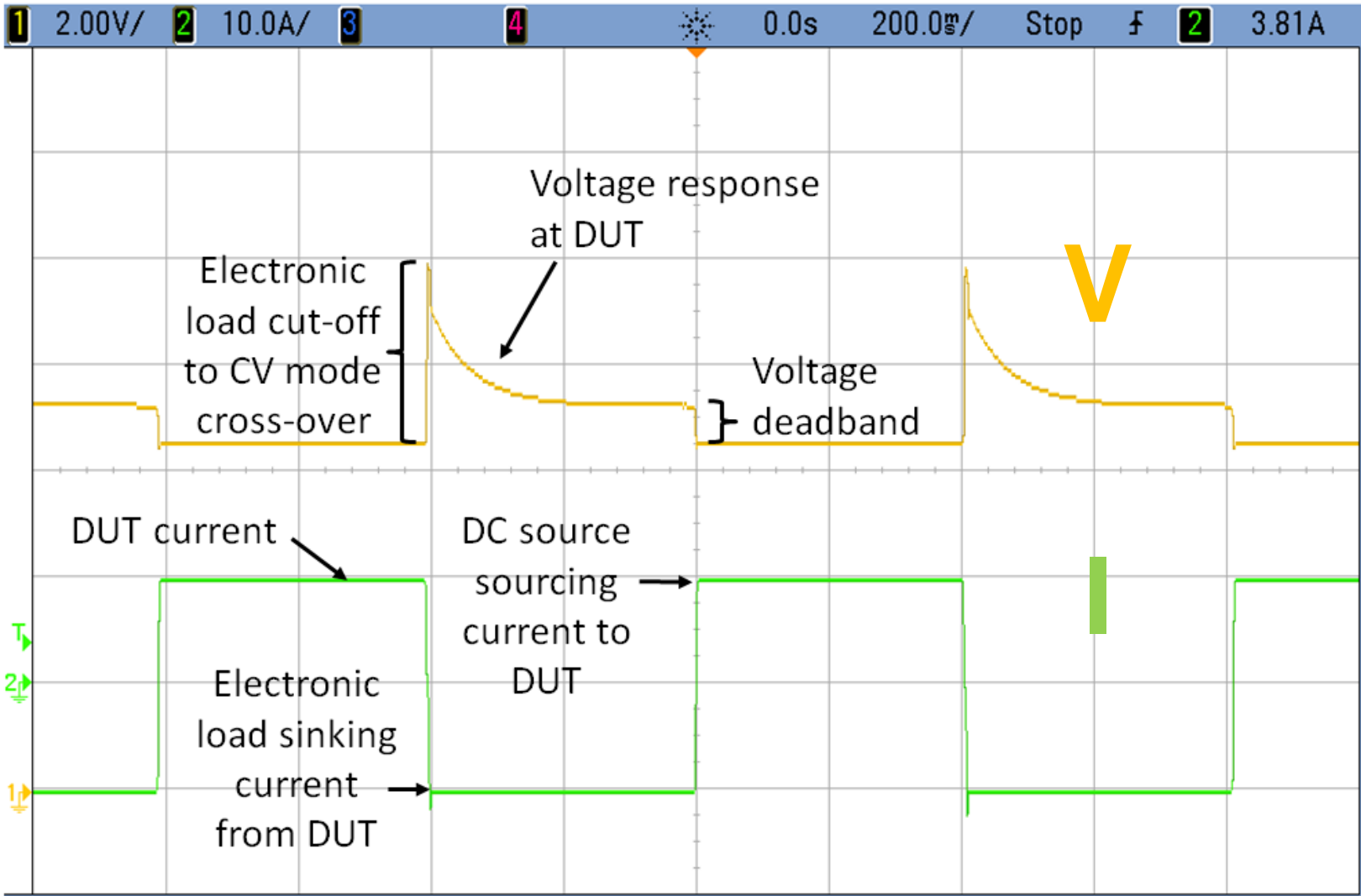Behavior of the solution under dynamic current conditions




Non-Overlapping Source-Sink Solution with Deadband

Disadvantages:

- Local sensing on DC source before blocking diode needed
- Deadband zone is high impedance
- Deadband voltage needs to be kept large due to diode voltage variance
- Programming is complex
- Electronic load mode cross-over transient compromises dynamic performance




Overlapping Source-Sink Operation

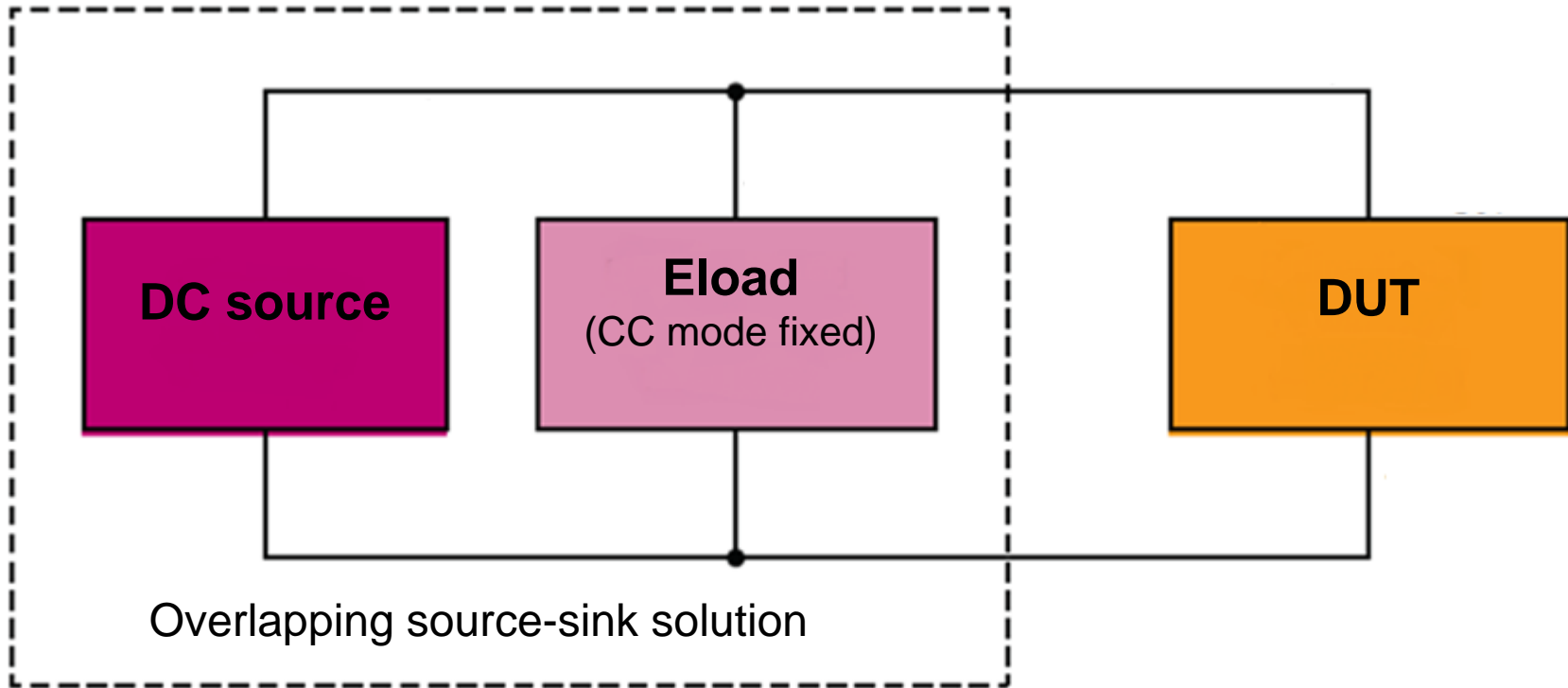

- This solution just uses a DC source and eload
- No deadband, can maintain constant voltage level
- Works better for batteries since CC conditions are easier to implement

Overlapping Source-Sink operation

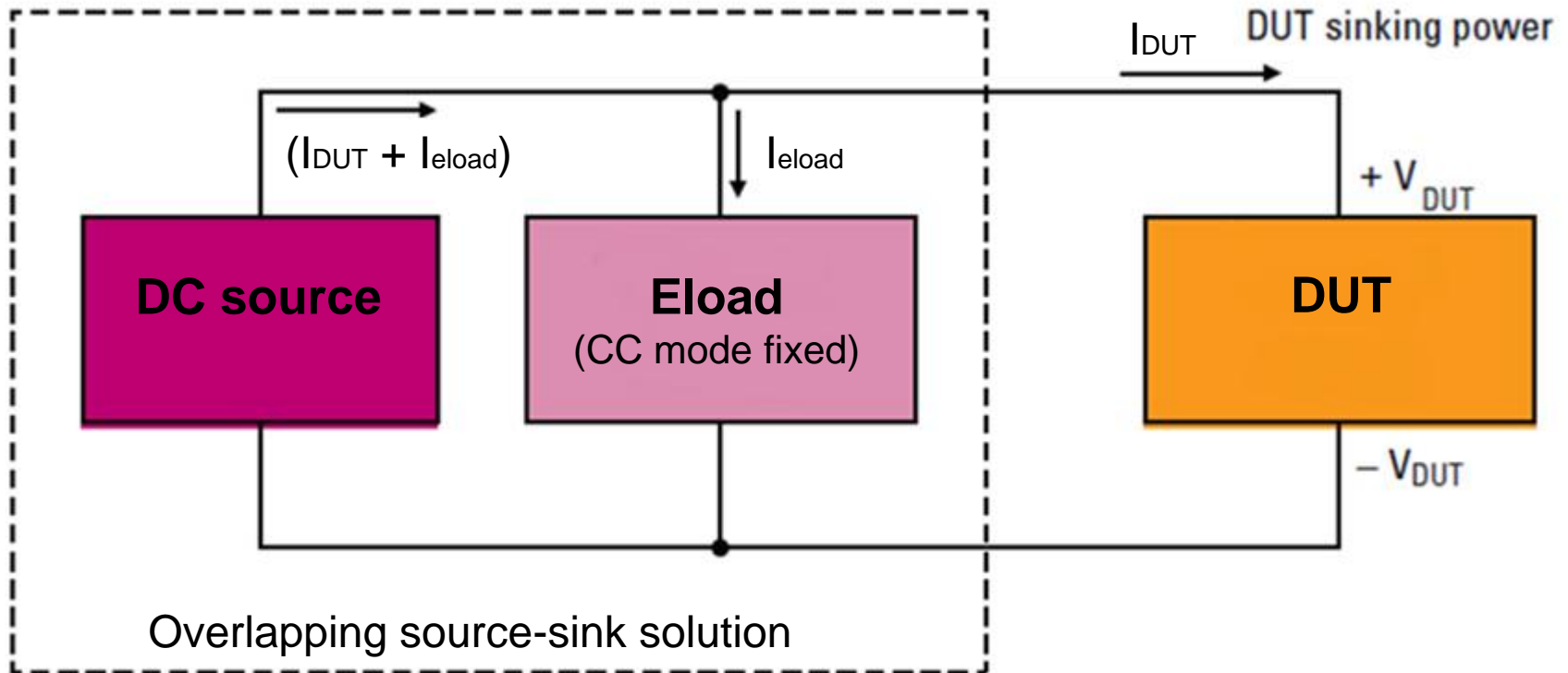
Overlapping solution sourcing power, DUT sinking power



- $V_{DUT} = V_{source}$
- DUT sinking power: $I_{source} = (I_{DUT} + I_{load})$
- DC source max current must be 2x DUT max sinking current

Overlapping Source-Sink operation

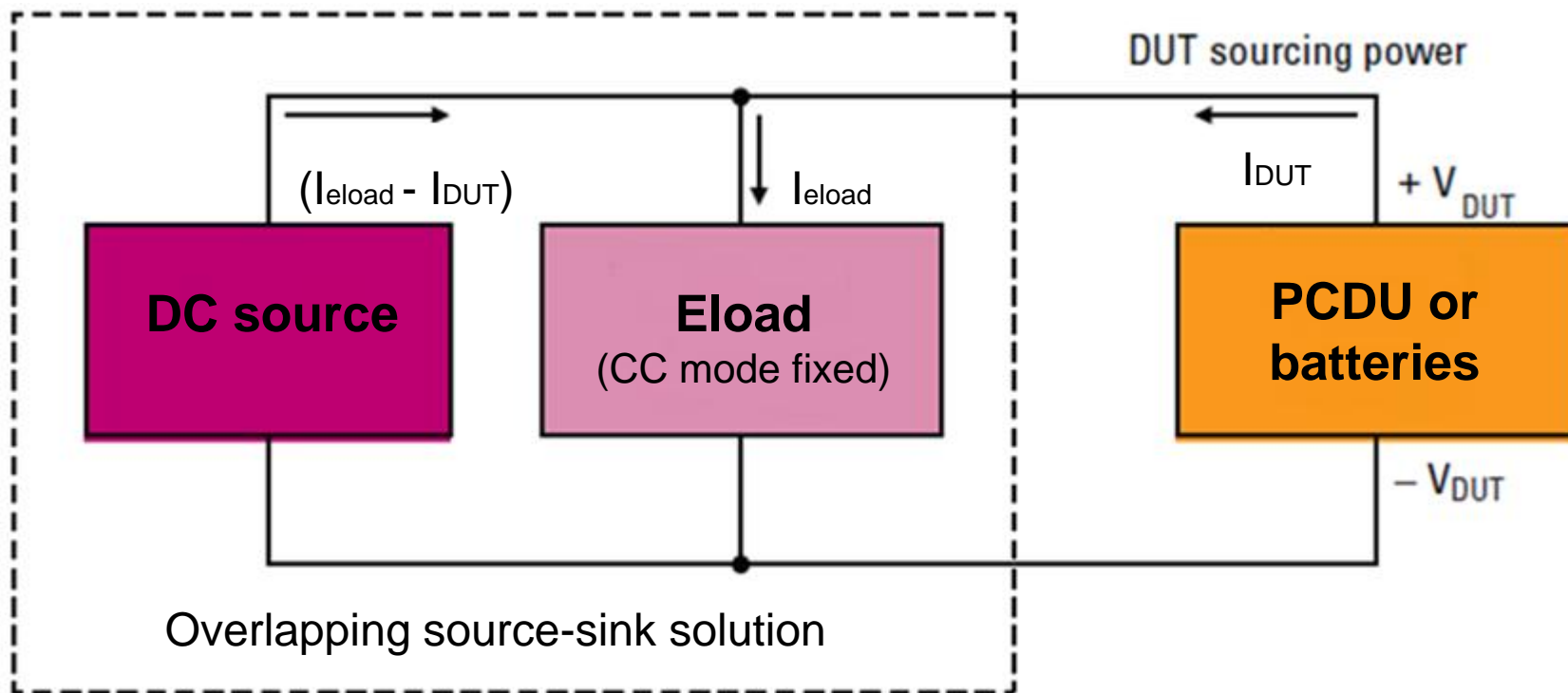
Overlapping solution sinking power, DUT sourcing power



- $V_{DUT} = V_{source}$
- DUT sourcing power: $I_{source} = (I_{load} - I_{DUT})$
- If the DC Source has downprogramming capabilities it could cause problems
- When testing devices such as BMS, may need to simulate battery Z for proper operation

Overlapping Source-Sink operation

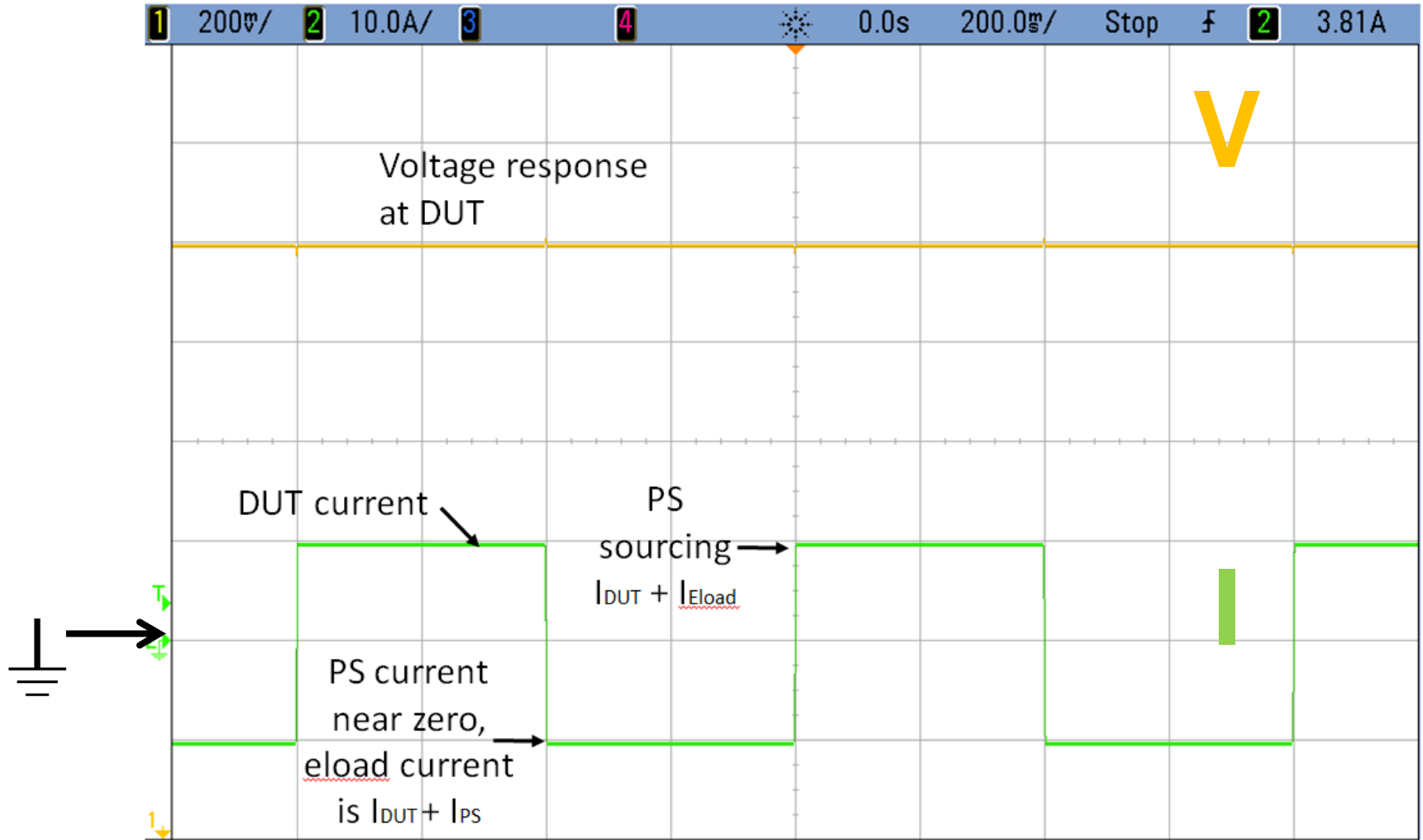Behavior of the solution under dynamic current conditions



Overlapping Source-Sink Operation

Advantages:


- Voltage response reasonably transient free by eliminating electronic load mode cross-over
- Since power supply is always sourcing power no more deadband

Disadvantages:

- Requires much larger DC source (2X for 100% sinking)
- Continuously dissipates large amount of power as waste
- Net DUT current is difference of DC source and electronic load readings. Reduces accuracy at low values
- May require additional custom hardware



Integrated Source-Sink Solution

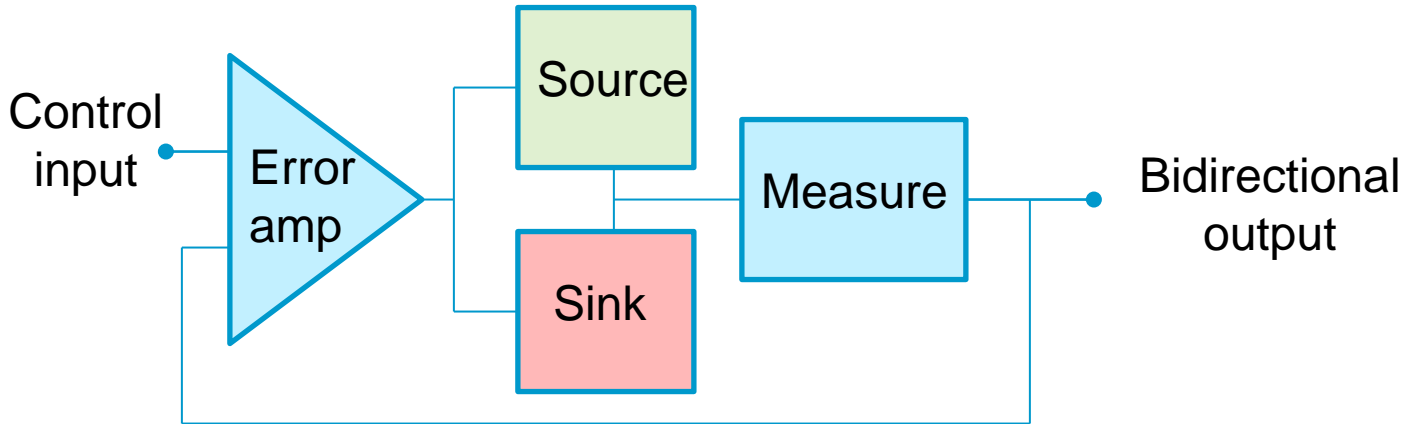

Integrating sourcing and sinking into a single instrument provides several advantages:

- Source and sink operation is controlled by **single regulation loop**
- Seamless transition between sourcing and sinking
- No need to dissipate large amounts of power
- Common measurement system for source and sink measurements

Integrated Source-sink Solution

The challenge is finding an integrated solution in the 1 kW and higher power range:

- Linear DC power supplies offer an architecture that supports two-quadrant operation, but become too large at high power levels
- Switching DC power supplies architecture does not easily support two-quadrant operation

Agilent found a way to address this test challenge based on a switching DC power supply architecture


Agenda

- The need for a source-sink test solution when testing bi-directional and regenerative power devices
- Solutions to address this need
 - Non-overlapping source-sink solution with deadband
 - Overlapping source-sink solution
 - Integrated source-sink solution
- New technologies for enabling integrated source-sink solution
- Conclusion




New Technologies for Enabling Integrated Solution

- Agilent has developed two patented technologies that enabled an integrated source-sink solution
 - Regulated by a single control loop
- This solution is built into a switching power supply architecture
- The technologies and story that led to this development:
 - Load-side down-programmer
 - Source-side down-programmer
 - Automatic down-programmer and external dissipater
- In the following slides we will take a look at these technologies and their progression

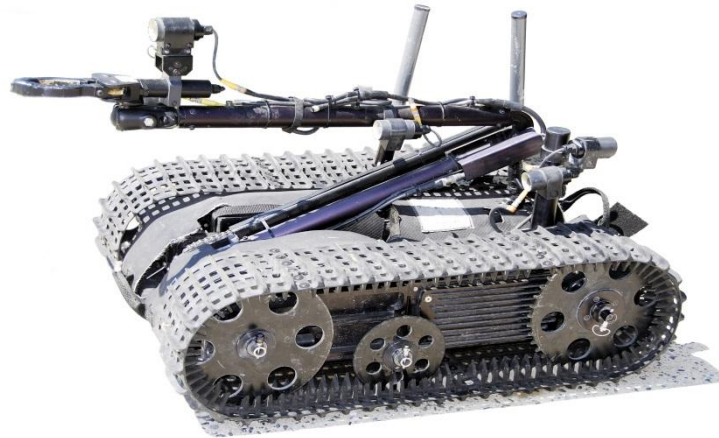

The Load-Side Down-Programmer

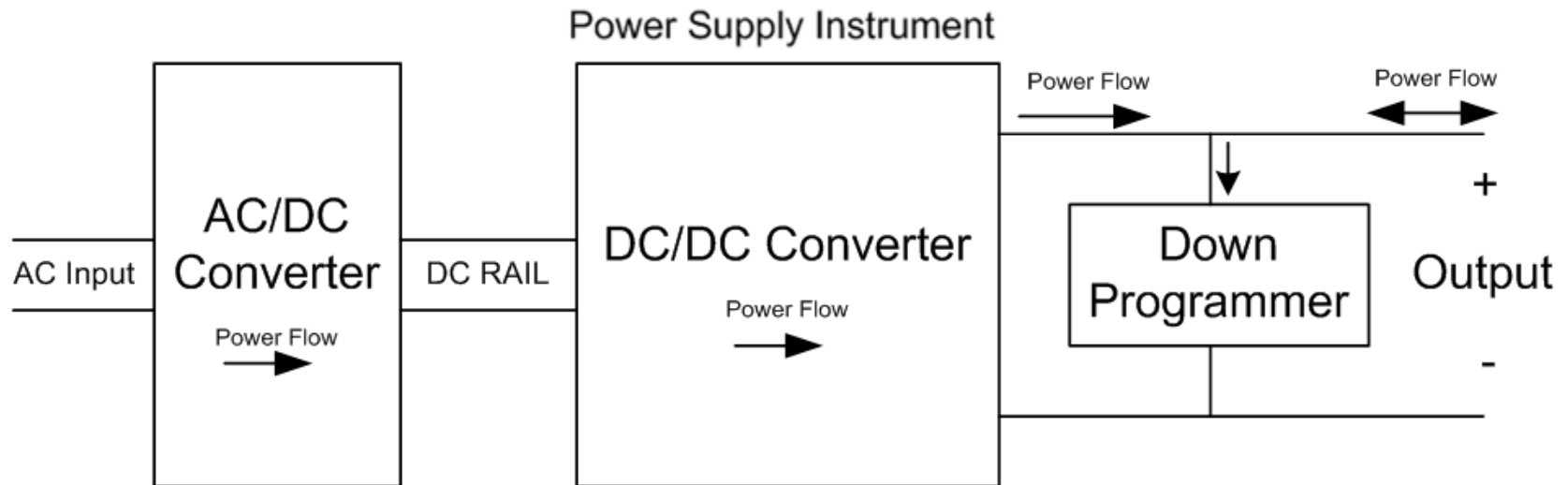
- Customer problem: needed method to discharge stored energy from the output filtering of the power supply as well as from the DUT input so output voltage could be quickly lowered.
- To solve this Agilent added active dissipative elements across the power supply's output, this subsystem became known as a down-programmer



Disadvantage: different down-programmer had to be designed for each unique voltage and power range.

Input-Side Down-Programmer

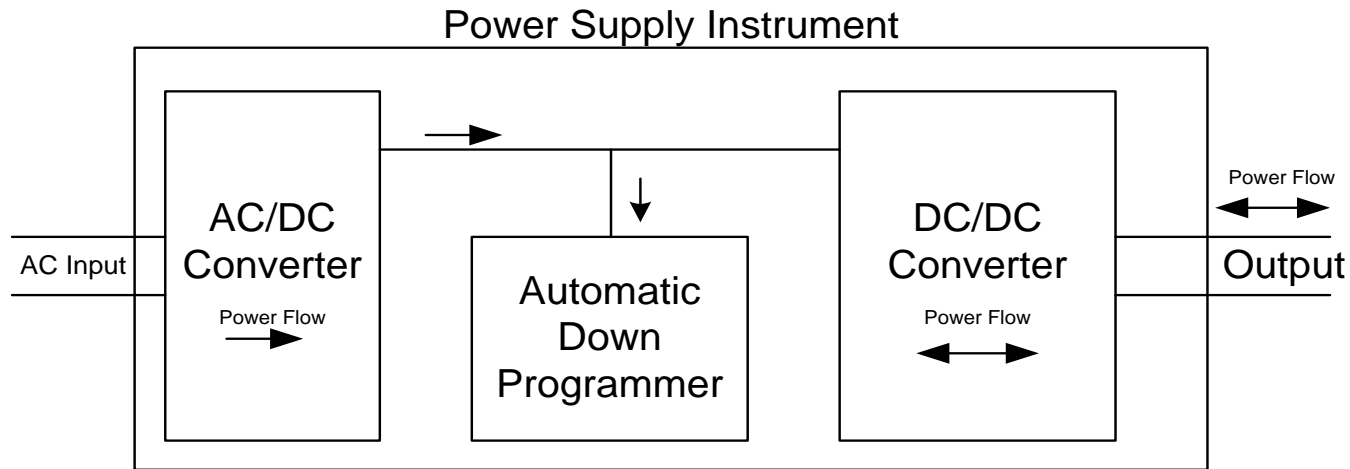- To avoid the disadvantage of load-side down-programmers, we made our DC to DC conversion stage bi-directional
- This allowed us to perform down-programming on the DC bus between the conversion stages where the DC level was common across many of our power supply families




- We developed the Automatic Down Programmer (ADP) to monitor the DC bus and sink current if the voltage went up
- The ADP is an Agilent only patented technology

Automatic Down-Programmer and External Dissipater

For our newest system power supply family:

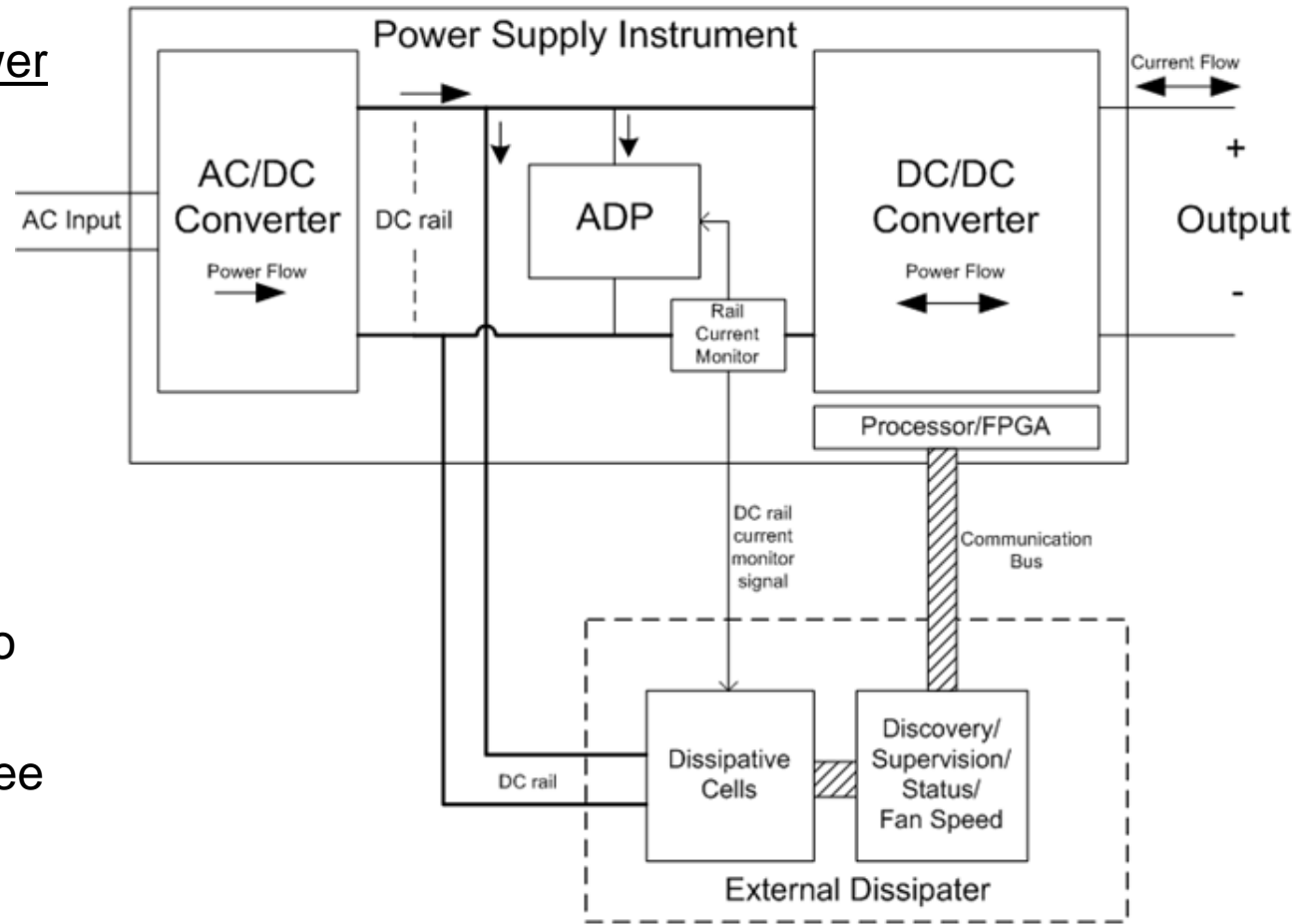- We made the ADP programmable
- ADP can sink 10% rated current of supply
- We added the patented External Dissipater (ED)
- The ED can extend the supply's sink capability to 100% full rated current
- The ED provides glitchfree two-quadrant operation



The patented ADP and ED technologies allow us to deliver a integrated source-sink solution for testing bi-directional and regenerative power devices

New Agilent Advanced Power System (APS)

DC power supplies with integrated sourcing and sinking



1000 W in 1U



2000 W in 2U



Parallel up to 10 kW

The APS has 2 performance levels

N6900 Series
DC Power Supply

Designed for ATE applications
where high performance is critical


N7900 Series
Dynamic DC Power Supply

Designed for ATE applications
where high-speed dynamic sourcing and
measurement is needed

APS N7909A Power Dissipater Unit



1000 W in 1U Full Rack

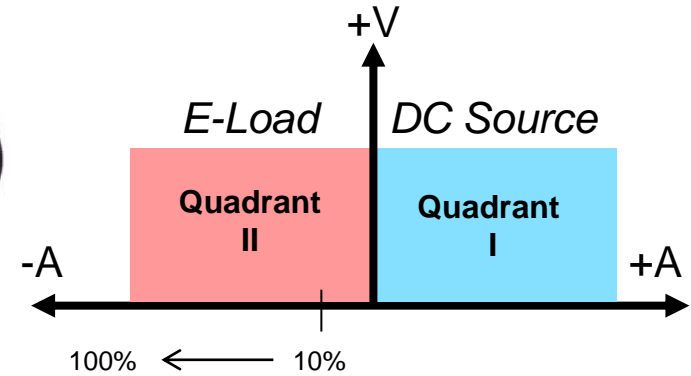


Add a Power Dissipater Unit to any APS power supply to provide continuous sink current at up to 100% with no limits on duty cycle

Provides seamless transition between source and sink. All control comes from the DC Source.

Add one dissipater for each 1 kW unit; add two dissipaters for each 2 kW unit


Gives you a DC Source and E-load in one setup with measurement and control of current flow in either direction (source or sink)

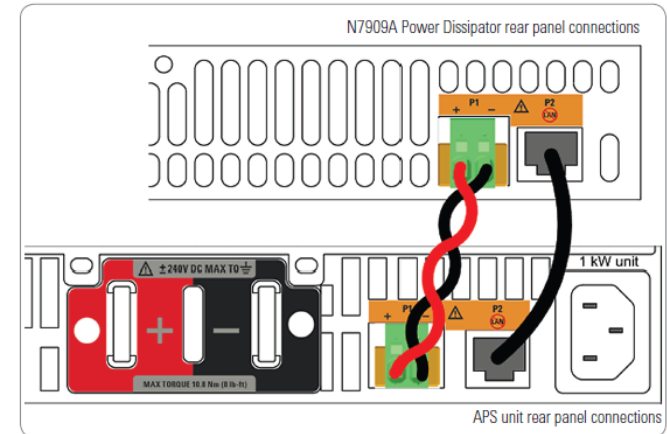Ideal for testing bi-directional and regenerative power devices



The APS as an Integrated Source-Sink Solution

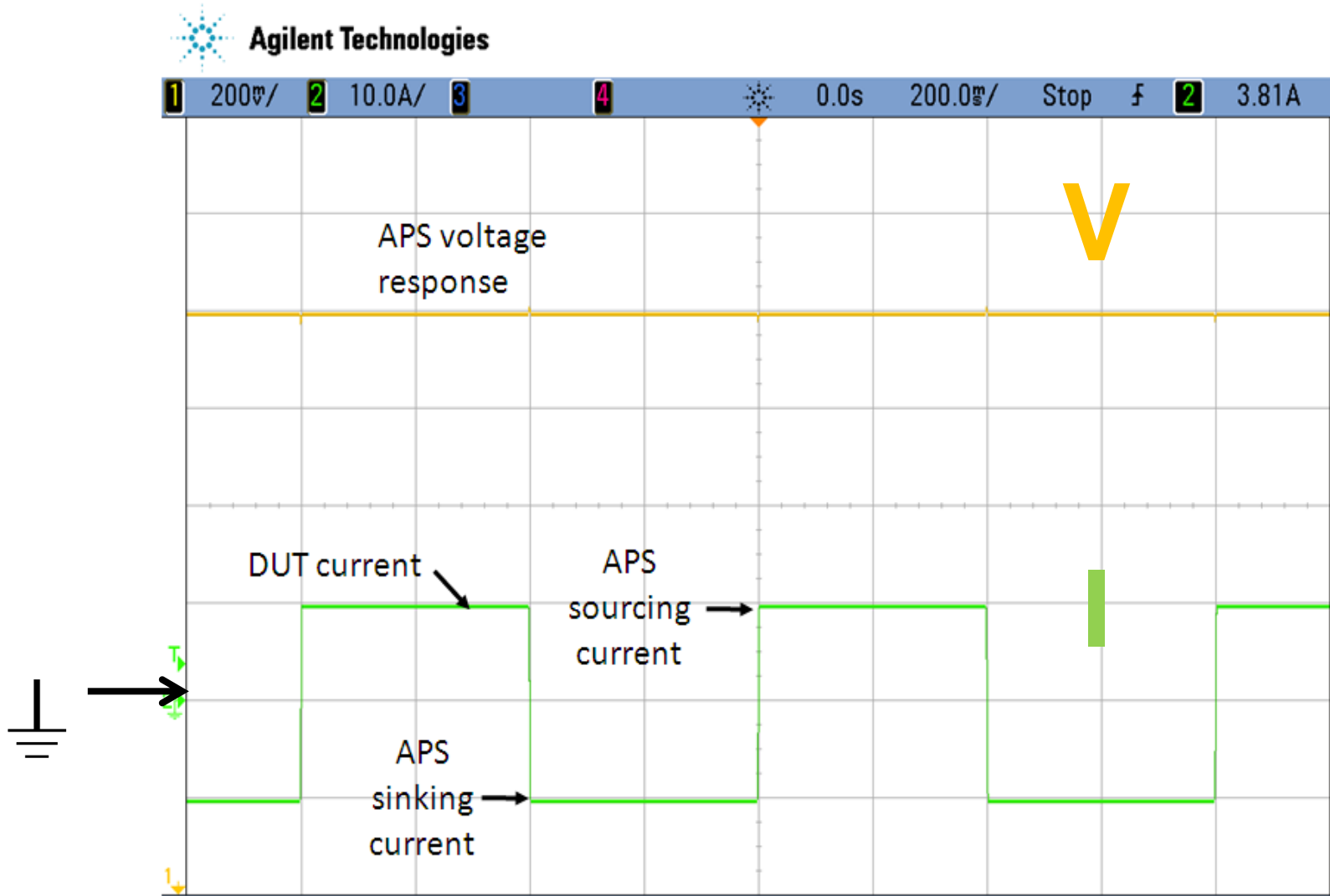Behavior of the solution under dynamic current conditions



The APS as an Integrated Source-Sink Solution

Benefits over other solutions:

- Source and sink operation is controlled by single regulation loop
- Seamless glitchfree transitions between source and sink operation
- No large amounts of power wasted
- Reduced hardware and software complexity
- Reduced hardware size and weight



Additional APS Capabilities that make it an Integrated Solution

- Meeting power storage measurements needs
 - 18 bit measurement capability captures: voltage, current, power, amp hour, and watt hour measurements
- Flexibility to adjust to your DUT's power needs
 - Built-in paralleling capability that ensures proper current sharing across units for maximum performance
 - Paralleling capability works whether current is being sourced or sinked
- Ensure your DUT is properly protected
 - Smart triggering system allows you to trigger off any measured level and create logical trigger expressions
 - Fast output speed to quickly react to OV and OC conditions
 - Built-in protection features such as watchdog timer, output relays, broken sense line detection, and more

Agilent N6900 Series DC power supplies

1 kW models

N6950A 9V, 100A

N6951A 20V, 50A

N6952A 40V, 25A

N6953A 60V, 16.7A

N6954A 80V, 12.5A

2 kW models

N6970A 9V, 200A

N6971A 20V, 100A



N6972A 40V, 50A

N6973A 60V, 33A

N6974A 80V, 25A

N6976A 120V, 16.7A

N6977A 160V, 12.5A

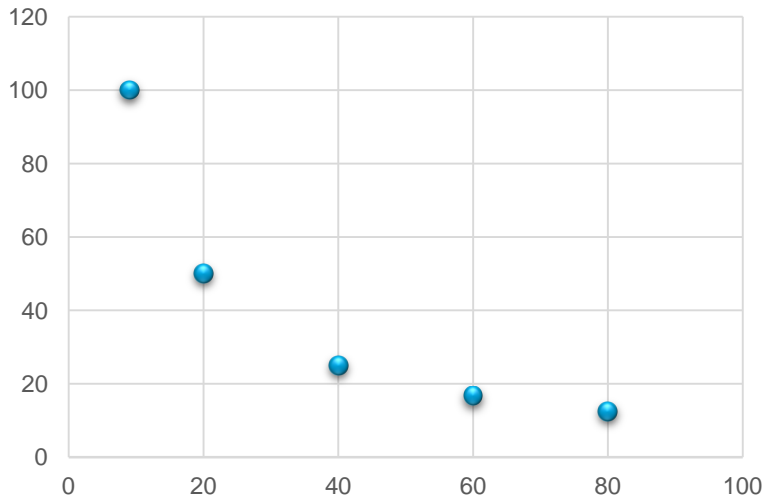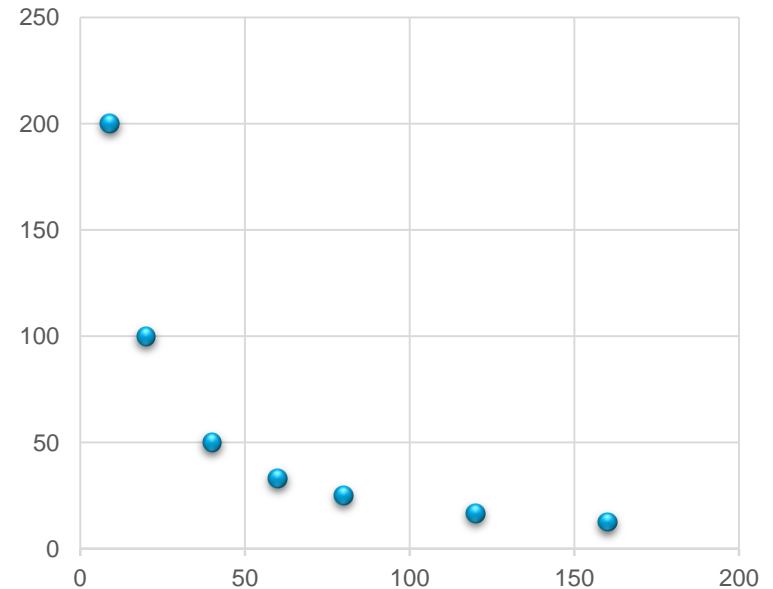

Agilent N7900 Series DC power supplies

1 kW models

N7950A 9V, 100A

N7951A 20V, 50A

N7952A 40V, 25A

N7953A 60V, 16.7A

N7954A 80V, 12.5A

2 kW models

N7970A 9V, 200A

N7971A 20V, 100A

N7972A 40V, 50A

N7973A 60V, 33A

N7974A 80V, 25A

N7976A 120V, 16.7A

N7977A 160V, 12.5A

Agenda

- The need for a source-sink test solution when testing bi-directional and regenerative power devices
- Solutions to address this need
 - Non-overlapping source-sink solution with Deadband
 - Overlapping source-sink solution
 - Integrated source-sink solution
- New technologies for enabling integrated source-sink solution
- Conclusion



Conclusion

Methods for creating a source-sink solution for testing bi-directional and regenerative power devices:

- Non-Overlapping Source-Sink Solution with Deadband
 - Disadvantage: complexity and does not provide constant voltage
- Overlapping source-sink solution
 - Disadvantage: complexity and uses a lot of power
- Integrated source-sink solution
 - Disadvantage: not many viable solutions available

New technologies for enabling integrated source-sink solution

- Automatic down-programmer: provides partial sinking capability
- External dissipater: provides optional full two quadrant operation
- Both these technologies can be found in the Advanced Power System N6900 and N7900 family

Questions?


Overcome your toughest power test challenges



with the Advanced Power System family
with **VersaPower**

-  Building a continuous source and load
-  Increasing test system throughput
-  Protecting against power related damage
-  Generating power transients
-  Characterizing inrush current
-  Characterizing dynamic current profiles
-  Properly powering on/off a DUT
-  Tracking power events for root-cause analysis
-  Maintaining output integrity under dynamic load conditions

Learn more about the test challenges the APS can help you overcome:
www.agilent.com/find/TestChallenges




Increasing test system throughput

Challenge: Reducing test time to increase test throughput is a continuous goal in high volume manufacturing

How the APS overcomes this:

- Fast output speed
- Output List mode
- Smart triggering
- Fast command processing



www.agilent.com/find/throughput



Building a continuous source and load


Challenge: Building a continuous source and load solution >500W for testing power storage related DUTs.

How the APS overcomes this:

- 2-quadrant operation
- V and I level triggering
- Fast output speed and response



www.agilent.com/find/SourceLoad




Protecting against power related damage


Challenge: Protecting costly DUTs from power related damage during test.

How the APS overcomes this:

- Smart triggering
- Fast output response
- Output disconnect relays
- Watchdog timer



www.agilent.com/find/ProtectDUT

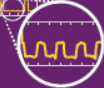


Characterizing dynamic current profiles


Challenge: Capturing the current profile of a DUT that has a large dynamic current range.

How the APS overcomes this:

- Current digitizer
- Seamless ranging
- Adjustable sample rate
- External logging



www.agilent.com/find/DynamicCurrent




Generating power transients


Challenge: Simulating power transients during test to ensure the DUT can standup to real world power conditions

How the APS overcomes this:

- AWG capability
- Step function capability
- High bandwidth mode



www.agilent.com/find/PowerTransients

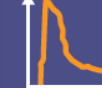


Characterizing inrush current


Challenge: Capturing the large current surge that occurs powering on DUTs with reactive elements at the input.

How the APS overcomes this:

- V and I digitizers
- Pre- and post-triggering
- Large measurement range



www.agilent.com/find/InrushCurrent




Maintaining output integrity under dynamic load conditions


Challenge: Maintaining a stable output voltage free of oscillations and voltage droop while under a very dynamic load

How the APS overcomes this:

- Fast transient response
- High and low output bandwidth modes
- Long test lead tolerance



www.agilent.com/find/PowerIntegrity




Tracking power events for root-cause analysis


Challenge: Tracking power events during test for root cause analysis if your expensive DUT is damaged during test.

How the APS overcomes this:

- Built-in Black Box Recorder
- Records voltage, current, power, trigger events and more



www.agilent.com/find/PowerTracking




Properly powering on/off a DUT

Challenge: Properly sequencing on multiple supplies and tuning slew rates to prevent damage.

How the APS overcomes this:

- Sequencing across mainframes
- Sequencing with N6700 mainframes
- Adjustable slew rate control



www.agilent.com/find/PoweringDUT